

Lecture 3

Converters I – Ideal Operation

1

Objectives

- Natural and Forced commutation
- To distinguish between
 - Inverters and
 - Converters
 - in the converter mode and
 - inverter mode
- Converters
 - Uncontrolled,
 - Half-controlled and
 - Fully-controlled converterswith different forms of supply, including
 - single-phase half-wave, full-wave
 - 3-phase
- To develop general equations describing many aspects of converter behaviour

Introduction

- Inverters & Converters are the circuits which exchange energy between an AC system and a DC system.

The two main cases:

- Systems with DC supply,
 - The circuit generate an AC source with voltage and frequency defined by the design of the circuit
 - The power flows from DC to AC and the circuit that performs this function is termed an inverter
- Systems with AC supply,
 - There exists an AC supply with fixed voltage and frequency (such as the mains supply) and
 - the circuit transfers power between this supply and a DC device with variable DC voltage defined by the design of the circuit

- The circuit that performs this function is termed a converter
- For a converter, the power flow may be from the AC supply to a DC load and this is referred to as a converter operating in the converter mode
- Alternatively, the power flow may be from a DC device back to the AC supply and this is referred to as a converter operating in the inverter mode

It is important to understand the difference between an 'inverter' and a 'converter operating in the inverter mode'

Some definitions

- For low and medium power applications - MOSFETs, bipolar transistors and gate turn-off thyristors
- For high power applications, such train motor control, thyristors have to be used
- Thyristor
 - Turn-on (i.e. made conductive)
 - gate pulse
 - Turn off
 - Reduce current flowing between the cathode and anode to below holding current
 - Maintain negative voltage for at least the turn-off time

Natural & Forced Commutation

- Commutation: Process of transferring conduction from one thyristor to another.
- AC supply of converter – when a thyristor is fired the change in the voltage of the supply since the previously conducting thyristor was fired satisfies the conditions for turn-off of the previously conducting thyristor – natural commutation.
- For inverter, no AC supply – special circuitry will have to be added to satisfy the conditions for switching off the thyristors forced commutation.


Converters

- Uncontrolled, half-controlled and fully-controlled
- Uncontrolled converter or rectifier:
 - Uses diodes only – output voltage determined solely by the magnitude of the AC supply
 - Energy can only be transferred from the AC supply to the DC load.
- Half-controlled converter:
 - Uses a combination of thyristors and diodes – able to control of the DC output voltage by varying the firing angle of the thyristors
 - Energy can only be transferred from the AC supply to the DC load
 - The half-controlled converter is cheaper than a fully-controlled converter of similar rating

- Fully-controlled Converter:
 - Uses only thyristors, with control of the DC output voltage determined by the thyristor firing angles
 - Operation can either be in
 - Converter (rectifying) mode with energy transferred from the AC supply to the DC load or
 - Inverting mode with energy transferred from the DC system to the AC supply
- Firing angle
 - defines the time at which a thyristor is fired,
 - Symbol α ; units radians or degrees

■ Zero reference

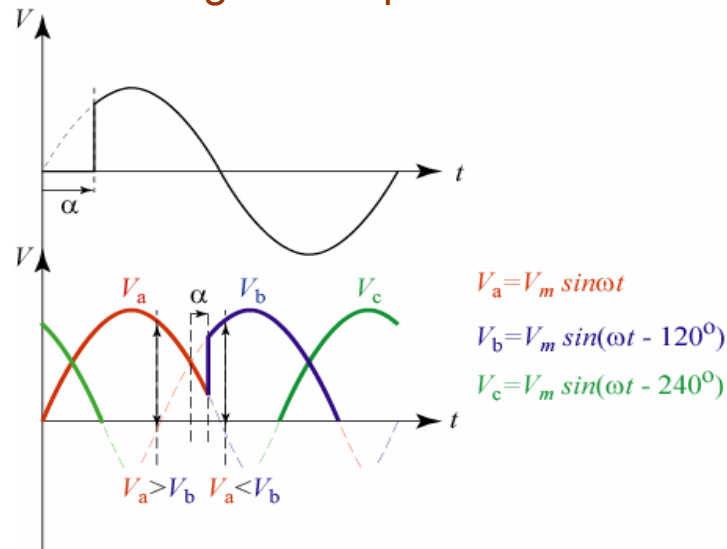- Point in the cycle of the AC waveform at which a diode would conduct if the thyristor is replaced by a diode
- Alternatively – the point in the cycle of the AC waveform when the voltage across the thyristor changes from negative to positive



■ Conduction angle

- it is the angle for which a switching device remains conducting with respect to the AC supply waveform period

■ Pulse number

- Number of discrete switching operations involving load transfer (commutation) between individual diodes or thyristors during the period covered by one cycle of the AC voltage waveform
- The pulse number is therefore directly related to the repetition period of the DC voltage waveform (or ripple)
- In general, the higher the pulse number, the lower the ripple amplitude

Converters with single-phase half-wave AC supply

- In a converter, diodes or switching devices, such as thyristors, are connected between the AC supply and the DC load
- AC supply voltage V can be described by:


$$V = V_m \sin \omega t$$

ω is frequency of supply and V_m is peak (or maximum) value.

ωt will occur frequently – convenient to give it the symbol θ

θ is angle with the units of radians which represents normalised time scale

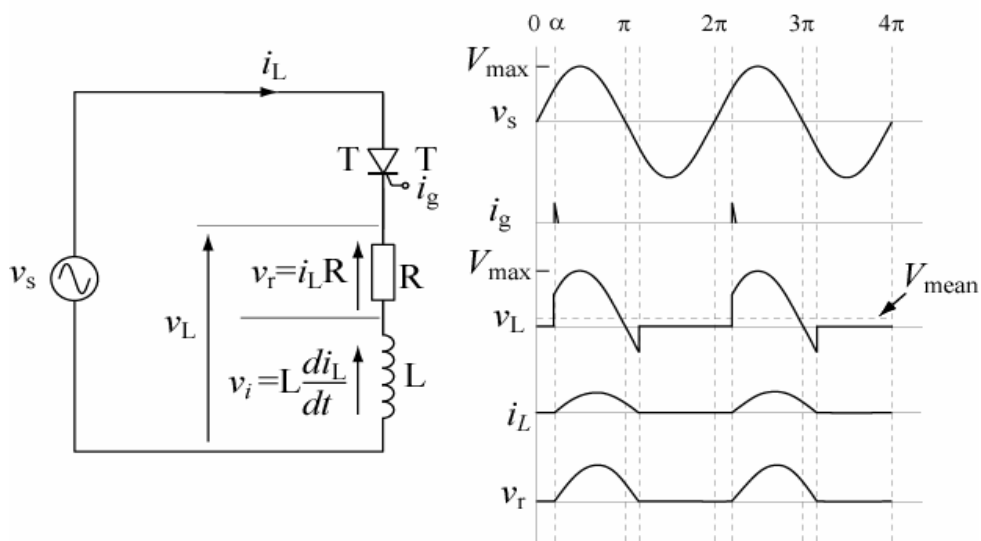- AC supply voltage and the load voltage waveforms



Converters with single-phase half-wave AC supply

- When the input voltage increases from zero to positive values, the load voltage remains at zero because the thyristor is non-conducting
- Load current waveform i_L is same as thyristor current:
 - The point on the AC waveform at which the thyristor is fired by a pulse applied to its gate terminal is defined by the firing angle α
- Once the thyristor fires (at $\theta = \alpha$), the thyristor behaves like a short-circuit and the load voltage follows the supply voltage

- Current then has form of half sine-wave which falls to zero at $\theta = \alpha + \pi$; it follows that the conduction angle is π
- With inductive load, the load voltage will reverse towards the end of conduction interval
- Thyristor only stops conducting when its current goes to zero (or below holding current) and a reverse voltage is maintained across it for at least the turn-off time
- Once the current has gone to zero, and the thyristor stops conducting, the load voltage will increase to zero, maintaining a negative voltage across the thyristor as required to complete the turn-off operation

Mean Voltage

- Determining the mean load voltage
 - The mean load voltage of a converter determines the power in the DC load
 - Mean load voltage is obtained by averaging the output voltage over a whole period of the output voltage waveform
 - The average is obtained by integrating to find the area under the voltage-time curve and then dividing by the range
 - Since the period of the output voltage waveform is the same as the period of the supply waveform we should integrate over a full supply period

- Integrate from $\theta = \alpha$ to $\theta = \alpha + 2\pi$
- Output voltage is zero after the thyristor ceases conduction, i.e. after $\theta = \alpha + \pi$
- Hence we can perform the integration over the range $\theta = \alpha$ to $\theta = \alpha + \pi$

$$V_{mean} = \frac{1}{2\pi} \int_{\alpha}^{\alpha+\pi} V_m \sin \theta d\theta$$

- Notice that although we are integrating over the conduction angle of π , when we divide by the range, we must use the full range of 2π

We can rewrite the equation to,

$$\begin{aligned}
 V_{mean} &= \frac{V_m}{2\pi} \int_{\alpha}^{\alpha+\pi} \sin \theta d\theta = \frac{V_m}{2\pi} [-\cos \theta]_{\alpha}^{\alpha+\pi} \\
 &= \frac{V_m}{2\pi} (-\cos(\alpha + \pi) - (-\cos \alpha)) \\
 &= \frac{V_m}{2\pi} (\cos \alpha + \cos \alpha) \\
 &= \frac{V_m}{\pi} \cos \alpha
 \end{aligned}$$

- α controls mean output voltage

- We can arbitrarily choose the starting time for the integration, but
- if a discontinuity in the output voltage waveform occurs in the middle of the integration range, then it will be necessary to carry out a separate integration for each part of the range
- This problem can be solved by choosing the integration range to begin and end with discontinuity so that only one integration is necessary.

Peak Reverse Thyristor Voltage

- Determining the peak reverse thyristor voltage
 - Can help to select thyristor can withstand this voltage
 - Voltage across thyristor equals difference between the supply voltage and load voltage
 - The peak reverse voltage occurs when the supply voltage is at its negative peak values and the output voltage is zero
 - Hence

$$|V_{rev-max}| = V_m$$

Uncontrolled Converter

- Single phase half-wave converter using a diode
- Thyristor in the converter is replaced by a diode – converter becomes uncontrolled converter
- Diode starts to conduct as soon as supply voltage becomes positive, i.e. at $\alpha = 0$
- Mean load voltage can be obtained by setting $\alpha = 0$ in controlled converter equations

$$V_{mean} = \frac{V_m}{\pi} \cos \alpha \Big|_{\alpha=0} = \frac{V_m}{\pi}$$


- And the peak reverse thyristor voltage

$$|V_{rev-max}| = V_m$$

- Uncontrolled converter sometimes referred to as rectifier
- The thyristor (or diode) current is equal to load current and
- thyristor has to have zero current to be able to switch off,
- Hence the load current will become zero for half of supply period
- Then we have the problem of non-constant load current, as ideal constant current is preferred.

Freewheeling diode

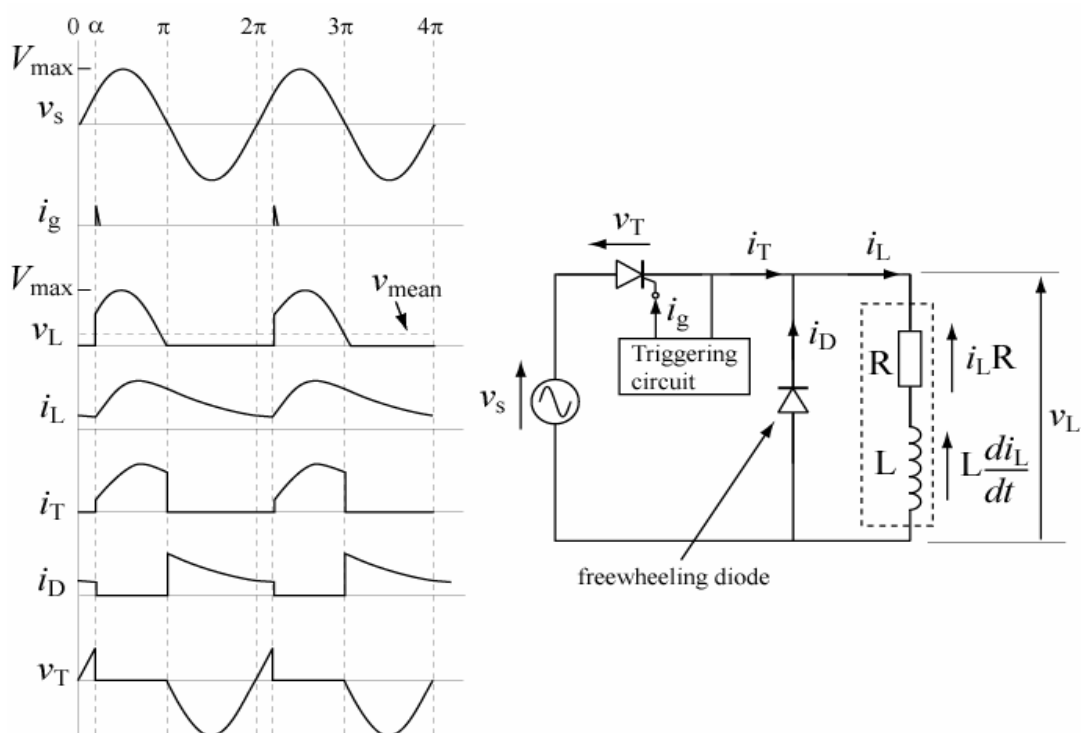- Introduce a freewheeling diode in parallel with the load



- Once supply voltage has increased above zero, thyristor may be fired.
- Load voltage then follows supply voltage; diode is reverse biased, it will take no current and have no effect at this stage.
- As soon as supply and load voltage fall to zero, further change in supply voltage will forward bias diode, which will come into a conductive state and act as short circuit preventing load voltage becoming negative
- In practice, load voltage will be negative of forward voltage drop of the diode, about -0.7 V, but this will be negligible compared to typical supply voltages used in power electronics, e.g. 100V

- When diode becomes conducting, load current will switch from thyristor to diode; hence, although the thyristor current becomes zero, as required for turn-off, load current can continue to flow in diode.
- When diode is conducting, small negative voltage of -0.7 V maintained at thyristor cathode completes its turn-off.
- Kirchoff's current law at output node defines currents relationship:

$$I_L = I_T + I_D$$

- When diode is conducting, current falls slightly as current maintained by inductive part of load dissipates energy in resistive part of load.

- Rate and extent of fall depends on load time constant:

$$\tau = \frac{L}{R}$$

- Freewheeling diode considerably reduces load current variation.
- Mean load voltage
 - Average converter output voltage over conduction interval
 - Conduction is from α to π , i.e. conduction period is $\pi - \alpha$

$$V_{mean} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta$$

- We can write the mean voltage as,

$$\begin{aligned} V_{mean} &= \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \theta d\theta = \frac{V_m}{2\pi} [-\cos \theta]_{\alpha}^{\pi} \\ &= \frac{V_m}{2\pi} (-\cos(\pi) - (-\cos \alpha)) \\ &= \frac{V_m}{2\pi} (1 + \cos \alpha) \end{aligned}$$

- For $\alpha = 0$ and is $V_{mean} = V_m/\pi$
 - For $\alpha = \pi$, we obtain $V_{mean} = 0$
- Compared with fully-controlled converter, we need larger changes in α to produce given change in V_{mean}

- Peak reverse thyristor voltage

Kirchoff's voltage law around the single loop of the converter circuit:

$$V_T = V_m - V_L$$

- Peak reverse voltage on thyristor is V_m , as before
- The diode voltage is the negative of the load voltage

- Half-wave single-phase converters have pulse number $p = 1$; period of output voltage ripple is equal to supply period
- Now consider converters with a pulse number of 2
- Center-tapped transformer converts single-phase supply to an effective 2-phase (bi-phase) supply
- Converters using such an arrangement are termed full-wave converters

Converters

With Single-phase Full-wave Uncontrolled


Uncontrolled converter using diodes

- Centre-tapped transformer produces anti-phase supply voltages V_1, V_2 :

$$V_1 = V_m \sin \theta$$

$$V_2 = -V_m \sin \theta = V_m \sin(\theta - \pi)$$

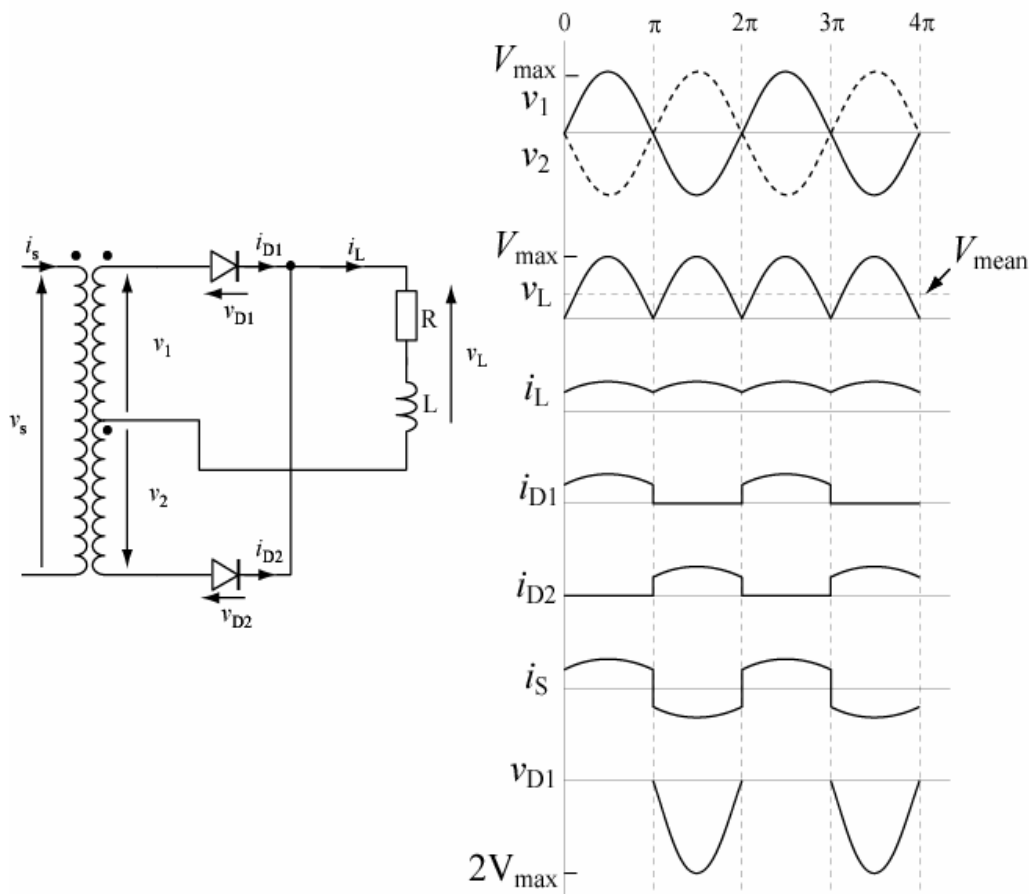- V_m is amplitude of bi-phase supply voltages and $\theta = \omega t$
- Assume the load is predominantly inductive.



- Principle of operation
 - Period of output ripple is half supply period; so pulse number is 2
- Current waveforms
 - Load current is fairly constant
 - Supply current is alternating, rather than unidirectional as for half-wave circuits
- Mean load voltage
 - averaging converter output voltage over period of output voltage ripple, namely $\theta = 0$ to π ;
 - Over this range, output voltage has form of positive half sine-wave:

$$V_{mean} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \theta d\theta$$

- We can write the mean voltage,

$$\begin{aligned}
 V_{mean} &= \frac{V_m}{\pi} \int_0^{\pi} \sin \theta d\theta = \frac{V_m}{\pi} [-\cos \theta]_0^{\pi} \\
 &= \frac{V_m}{\pi} (-\cos(\pi) - (-\cos 0)) \\
 &= \frac{V_m}{\pi} \cdot 2 \\
 &= \frac{2V_m}{\pi}
 \end{aligned}$$

- Peak reverse diode voltage
 - Kirchoff's voltage law to loop of converter circuit

$$V_{D1} = V_1 - V_2 + V_{D2}$$

- When D_1 is reverse biased, D_2 is forward biased and $V_{D2} = 0$
- Hence


$$V_{D1} = V_1 - V_2$$

- The peak reverse voltage on the diode is $2V_m$

Converters With Single-phase Full-wave Full-controlled

Full-wave converter using thyristors

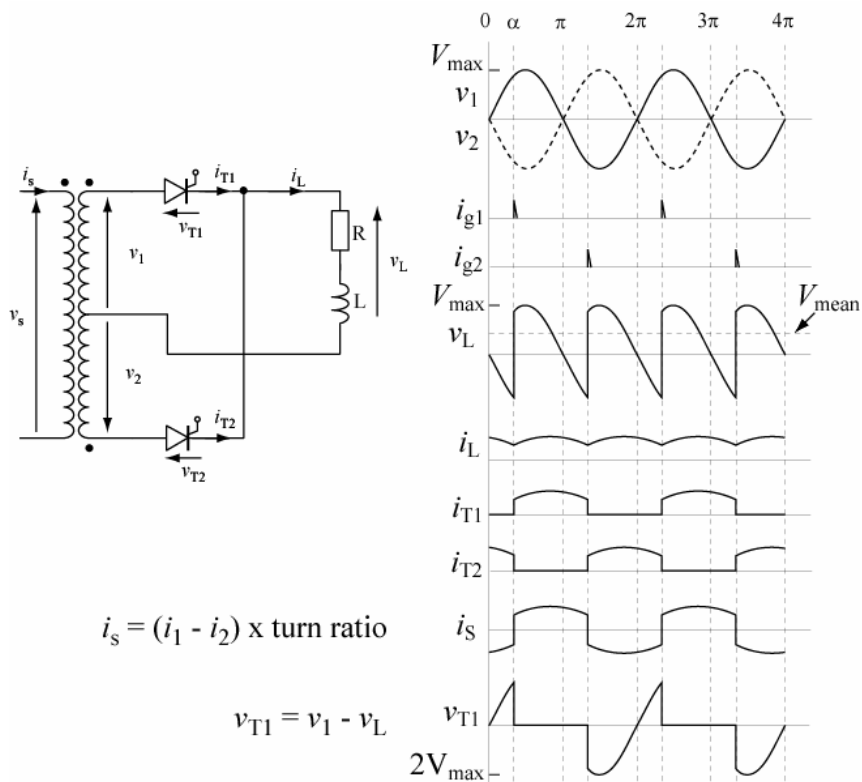- Assume load which is predominantly inductive
- Firing angle α for each thyristor define with respect to point on wave when diode would commence conduction
- Conduction for each thyristor is from $\theta = \alpha$ to $\theta = \alpha + \pi$; therefore conduction angle is π
- Period of output ripple is half supply period; so pulse number is 2.



■ Applying Kirchoff's current law:

$$I_L = I_{T1} + I_{T2}$$

■ Load current is relatively constant and supply current is alternating

■ Mean load voltage

- Average converter output voltage over its period, from $\theta = \alpha$ to $\alpha + \pi$:

$$\begin{aligned}
 V_{mean} &= \frac{V_m}{\pi} \int_{\alpha}^{\alpha+\pi} \sin \theta d\theta = \frac{V_m}{\pi} [-\cos \theta]_{\alpha}^{\alpha+\pi} \\
 &= \frac{V_m}{\pi} (-\cos(\alpha + \pi) - (-\cos \alpha)) \\
 &= \frac{2V_m}{\pi} \cos \alpha
 \end{aligned}$$

- Maximum mean load voltage of $2V_m/\pi$ is obtained for $\alpha = 0$
- If we set the firing angle α to 0, this is equivalent to replacing the thyristors by diodes and it can be confirmed that the mean load voltage becomes $2V_m/\pi$, which agrees with the result obtained in the previous section
- For $\alpha = \pi/2$, mean load voltage falls to zero
- Peak reverse thyristor voltage
 - Applying Kirchoff's voltage law to the converter circuit, we can write the thyristor voltage (for T_1):

$$V_{T1} = V_1 - V_2 + V_{T2}$$


- When T_1 is reverse biased, then T_2 is forward biased and $V_{T2} = 0$

$$V_{T1} = V_1 - V_2$$

- It can be seen that the peak reverse voltage on each thyristor is $2V_m$
- Next consider another type of converter with a pulse number of 2 which we refer to as the bridge converter
- Replace the transformer by using additional switching devices

Bridge converters with single-phase AC supply

Fully-controlled bridge converter

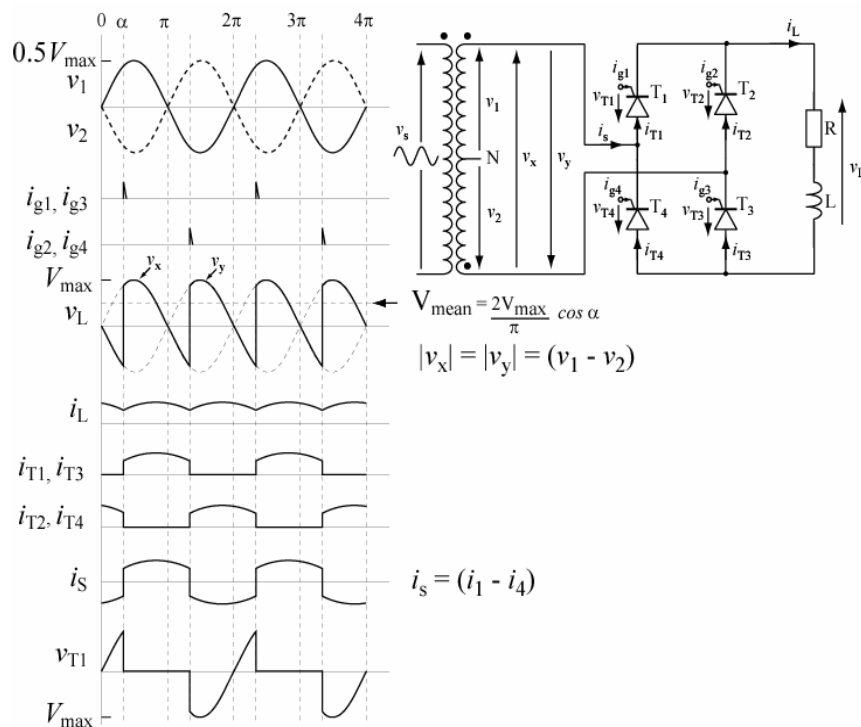

■ Circuit diagram

- Positive (upper) terminal of load is connected to both terminals of AC supply by forward directed thyristors
- Negative (lower) terminal of load is connected to both terminals of AC supply by reverse directed thyristors
- Supply and load do not share common ground

■ Principle of operation

Positive half cycle of AC supply voltage is V

- thyristors T_1 and T_3 fired together – AC supply voltage is $+V$

Negative half cycle of AC supply voltage

- thyristor T_2 and T_4 are fired – AC supply voltage is $-V$

- We effectively have two supply voltages (+V and – V) with load voltage tracking first one and then the other as the thyristors switch:
 - Output voltage wave form is identical to that for fullwave fully-controlled converter
- Conduction for each thyristor from $\theta = \alpha$ to $\theta = \alpha + \pi$
- Conduction angle = π ;
- Pulse number = 2

- These waveforms are identical to those for the fullwave converter
- Mean load voltage
Averaging converter output voltage over period of output voltage, from $\theta = \alpha$ to $\alpha + \pi$

$$V_{mean} = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} V_m \sin \theta d\theta$$

Same expression as for fullwave converter:

$$V_{mean} = \frac{2V_m}{\pi} \cos \alpha$$

Maximum mean output voltage obtained for $\alpha = 0$ and is $2V_m/\pi$; mean output voltage of zero obtained for $\alpha = \pi/2$

- Peak reverse diode voltage

Apply KVL to converter circuit; write thyristor voltage (for T_1):

$$V_{T1} = V_1 + V_{T2}$$


- When T_2 is forward biased,

$$V_{T2} = 0$$

$$V_{T1} = V$$

- Maximum reverse voltage on thyristor (T_1) is V_m

Half-controlled bridge converter

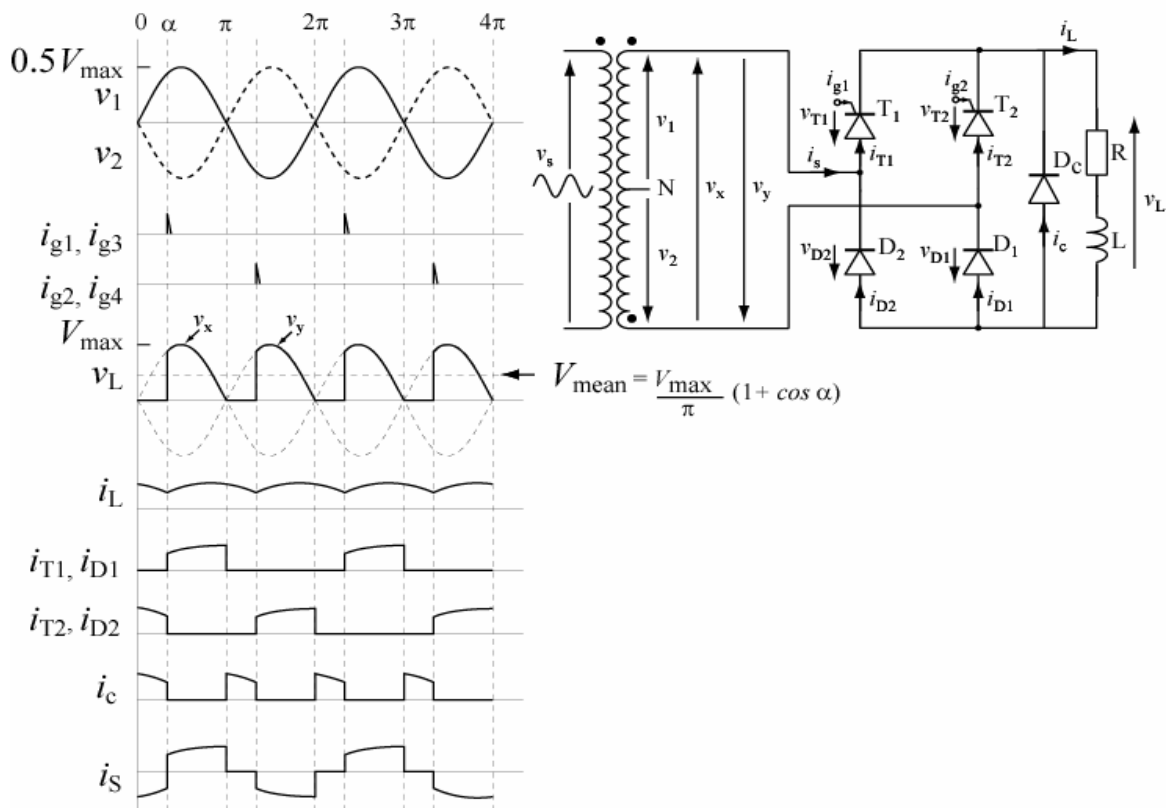

- In fully-controlled bridge converter, replace thyristors T_3 and T_4 by diodes (D_1 and D_2) and introduce freewheeling diode.
- Principle of operation
 - Positive half cycle of AC supply voltage V – T_1 is fired and current returns to lower terminal of AC supply via D_1
 - Negative AC supply half cycle $-T_2$ is fired and current return is via D_2
 - When supply voltage falls to zero, freewheeling diode will conduct; load current switches from thyristor to diode and thyristor is extinguished

- Pulse number is 2
- Current fall when diode conducts depends on load time constant $\tau = L/R$
- Mean load voltage
 - Thyristor conduction interval from $\theta = \alpha$ to π ;
- Conduction angles, thyristors: $\pi - \alpha$; diode: α
- Average output voltage over the period of output voltage i.e. π
- Load voltage zero from $\theta = \pi$ to $\pi + \alpha$, limits of integration from α to π :

$$\begin{aligned}
 V_{mean} &= \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{\pi} [-\cos \theta]_{\alpha}^{\pi} \\
 &= \frac{V_m}{\pi} (-\cos(\pi) - (-\cos \alpha)) \\
 &= \frac{V_m}{\pi} (1 + \cos \alpha)
 \end{aligned}$$

- Maximum mean output voltage for $\alpha = 0$ and is $2V_m/\pi$,
- Minimum mean output voltage zero obtained for $\alpha = \pi$
- For half-controlled converter, we need larger changes in α to produce a given change in V_{mean}

- Peak reverse thyristor and diode voltages
Kirchoff's voltage law for converter circuit:

$$V_{T1} = V + V_{T2}$$

When T_2 is forward biased $V_{T2} = 0$; hence:

$$V_{T1} = V$$

The maximum reverse voltage on the reverse biased thyristor (T_1) is V_m

By a similar argument, peak reverse voltage for diodes is also V_m

Example

A highly inductive load (i.e. with constant current) is supplied from a 240V 50Hz (RMS) single-phase AC supply via a fully-controlled and a half-controlled bridge

- Compare load voltages for firing angles α of 30° and 90°

Solution

AC voltages are usually specified in RMS Volts, so it is necessary to multiply by $\sqrt{2}$ to obtain peak voltage:

- Fully-controlled bridge

$$V_{mean,30^\circ} = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times 240 \times \sqrt{2}}{\pi} \cos 30^\circ = 187.1V$$

$$V_{mean,90^\circ} = \frac{2 \times 240 \times \sqrt{2}}{\pi} \cos 90^\circ = 0V$$

- Half-controlled bridge

$$V_{mean,30^\circ} = \frac{V_m}{\pi} (1 + \cos \alpha) = \frac{240 \times \sqrt{2}}{\pi} (1 + \cos 30^\circ) = 201.6V$$

$$V_{mean,90^\circ} = \frac{240 \times \sqrt{2}}{\pi} (1 + \cos 90^\circ) = 108.0V$$


Greater sensitivity of control obtained with fully-controlled converter

Converters with 3-phase AC supply

- Single-phase converters limited to powers of few kiloWatts
- For higher power levels – converters based on 3-phase systems 3-phase supply:
 - Higher pulse numbers
 - Reduced load voltage ripple and load current ripple
- 3 lines of 3-phase supply may be connected to load in two ways:
 - Star-connection and
 - delta-connection


Star Connection

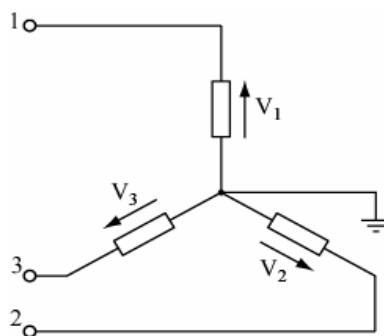- In star arrangement, each load impedance is connected to supply line at one end and to common ground at other end;
- Voltages V_1 , V_2 and V_3 referred to as phase voltages



Delta Connection

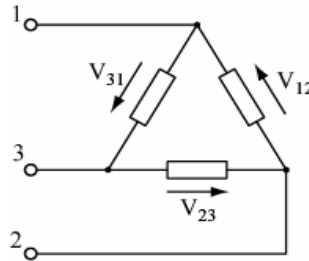- In delta arrangement, each load is connected between different pairs of supply lines and none is connected to common ground;



- Delta load voltages, V_{12} , V_{23} and V_{31} referred to as line voltages (short for line-to-line) and are differences of phase voltages:

$$V_{12} = V_1 - V_2$$

$$V_{23} = V_2 - V_3$$

$$V_{31} = V_3 - V_1$$

Phase Voltages

- Phase voltages

3 phase voltages in 3-phase supply have same maximum amplitude V_m and 120° ($2\pi/3$ radians) phase differences:


$$V_1 = V_m \sin \theta$$

$$V_2 = V_m \sin\left(\theta - \frac{2\pi}{3}\right)$$


$$V_3 = V_m \sin\left(\theta - \frac{4\pi}{3}\right)$$

where $\theta = \omega t$, V_m is peak phase voltage

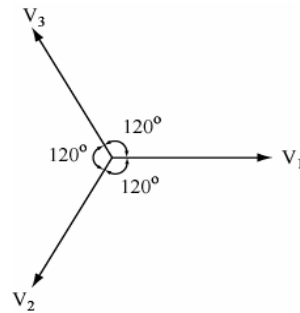- Phase voltages may be represented as vectors:



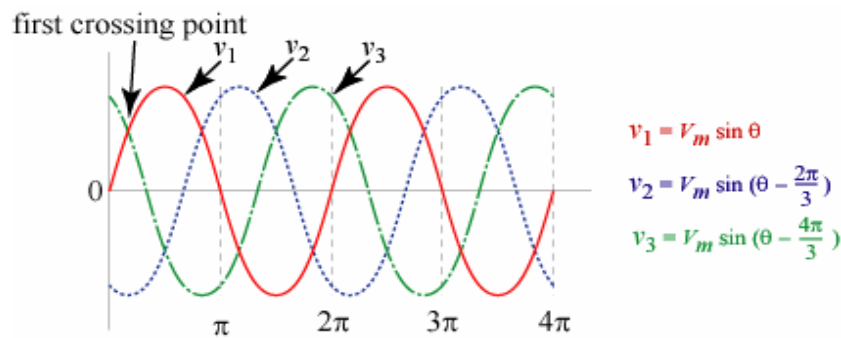- V_1 , V_2 and V_3 may be plotted against θ (or t):



- For the first crossing (of V_1 and V_3), we may write:

$$\begin{aligned} \sin \theta &= \sin\left(\theta - \frac{4\pi}{3}\right) = \sin \theta \cos \frac{4\pi}{3} - \cos \theta \sin \frac{4\pi}{3} \\ &= -\frac{1}{2} \sin \theta - \frac{\sqrt{3}}{2} \cos \theta \\ \frac{3}{2} \sin \theta &= \frac{\sqrt{3}}{2} \cos \theta \\ \tan \theta &= \frac{1}{\sqrt{3}} \\ \theta &= \frac{\pi}{6} = 30^\circ \end{aligned}$$

- Crossing-points are $\pi/6$ radians or 30° after the point where one of the waveforms crosses zero

Line Voltage

■ Line voltages

Line voltages are the voltages existing between pairs of phase voltages:

$$V_{12} = V_1 - V_2 \quad V_{23} = V_2 - V_3 \quad V_{31} = V_3 - V_1$$

Substituting for V_1 and V_2 , we obtain:


$$\begin{aligned} V_{12} &= V_1 - V_2 \\ &= V_m \sin \theta - V_m \sin \left(\theta - \frac{2\pi}{3} \right) \\ &= 2V_m \cos \left(\theta - \frac{\pi}{3} \right) \sin \frac{\pi}{3} \\ &= \sqrt{3}V_m \sin \left(\theta + \frac{\pi}{6} \right) \end{aligned}$$

■ In a similar way, we obtain:

$$V_{23} = \sqrt{3}V_m \sin \left(\theta - \frac{\pi}{2} \right) \quad V_{31} = \sqrt{3}V_m \sin \left(\theta + \frac{5\pi}{6} \right)$$


■ Line voltages

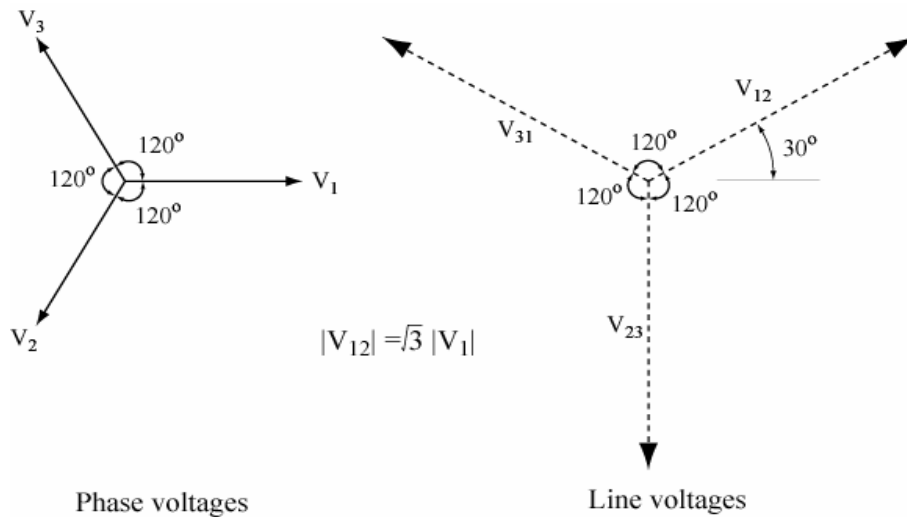- Magnitude $\sqrt{3}$ times larger than phase voltages
- Each differs in phase from next one by 120° ($2\pi/3$ radians)
- Complete set rotated by 30° ($\pi/6$ radians) with respect to phase voltages:



■ Important to be aware of whether specified voltage of a 3-phase supply is phase voltage or line voltage

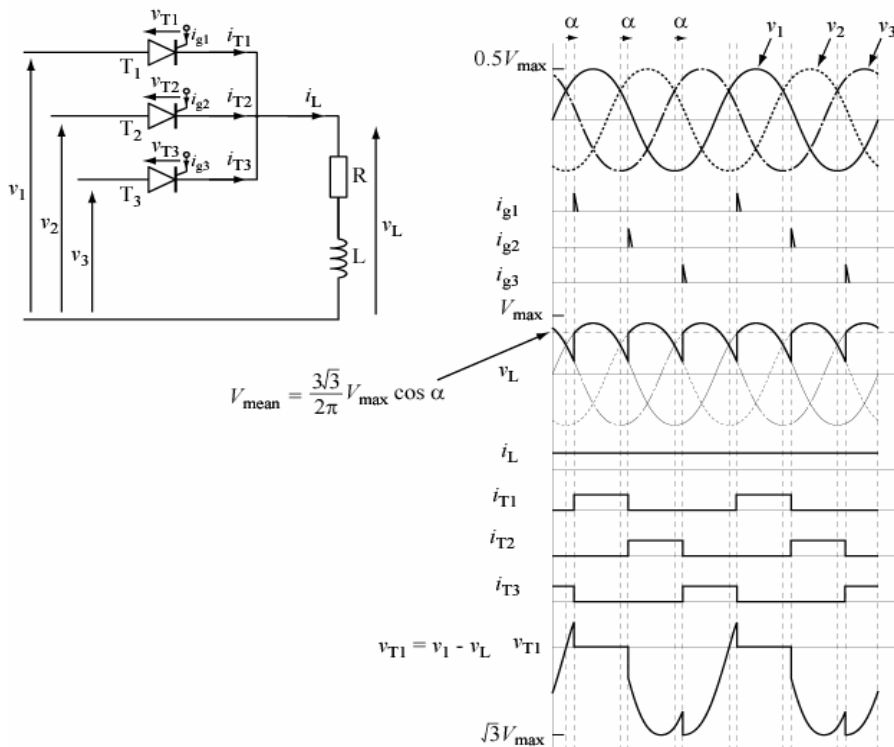3-phase half-wave fully-controlled converter



■ Assume load is heavily inductive

- Principle of operation
 - firing angle is about 40° :
- Assume T_1 conducting and load voltage following V_1 ; next thyristor to be fired is T_2
 - Voltage across T_2 :

$$V_{T_2} = v_2 - V_L = v_2 - v_1$$
 - The earliest instant when we can fire T_2 is when V_{T_2} becomes positive, i.e. when v_2 crosses v_1 (with v_2 rising and v_1 falling)
 - If T_2 was diode, this is point when it would begin conducting so it is zero reference point for firing angle α
 - Latest point T_2 may be fired is π radians later, when v_1 and v_2 cross again (with v_1 rising and v_2 falling) and voltage across T_2 changes sign again
 - Each thyristor conducts from $\theta = \alpha$ to $\alpha + 2\pi/3$;
 - Conduction angle = $2\pi/3$
 - Pulse number is 3 since period of voltage ripple is $1/3^{\text{rd}}$ supply period

- Load current
 - It can be practically constant with very little ripple
 - Each thyristor conducts for $1/3^{\text{rd}}$ of the supply period
 - Supply current in each phase is equal to current in the thyristor it is feeding; it follows that supply current in each phase is unidirectional and flows also for $1/3^{\text{rd}}$ of supply period
 - In practice, it is desirable that supply currents are truly alternating (bi-directional); ways of achieving this will be considered later
- Mean load voltage
 - Since period of output voltage is $2\pi/3$, this will be integration range

- To avoid multiple integrations, we integrate from discontinuity to discontinuity
- We can write this

$$\begin{aligned}
 V_{mean} &= \frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} V_m \sin \theta d\theta \\
 &= \frac{3V_m}{2\pi} \left[-\cos \theta \right]_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} \\
 &= \frac{3V_m}{2\pi} \left(-\cos \left(\frac{5\pi}{6} + \alpha \right) - -\cos \left(\frac{\pi}{6} + \alpha \right) \right) \\
 &= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha
 \end{aligned}$$

- Maximum mean output voltage obtained for $\alpha = 0$ and is $3\sqrt{3}V_m/(2\pi)$
- For $\alpha = \pi/2$, mean load voltage falls to zero
- **Peak reverse thyristor voltage**
 - Apply Kirchoff's voltage law to converter circuit:
Thyristor T_1 voltage:

$$V_{T1} = V_1 - V_L$$
 - When T_1 is non-conducting, T_2 first conducts and then T_3 conducts
 - When T_2 conducts: $V_L = V_2$ and $V_{T1} = V_1 - V_2 = V_{12}$
 - When T_3 conducts: $V_L = V_3$ and $V_{T1} = V_1 - V_3 = V_{13}$
 - Hence, voltage across T_1 is equal to two line voltages, V_{12} and V_{13}
 - Maximum reverse voltage therefore = maximum line voltage = $-\sqrt{3}V_m$

■ Device Ratings

Power semiconductor devices limited by ratings – define operating boundaries within which device guaranteed to operate safely and reliably

- Peak, average and RMS currents
- Peak forward and reverse voltages
- Rates of change of device current and voltage
- Device junction temperatures

We now determine RMS values of thyristor currents

■ RMS values of voltages and currents

- Constant DC voltage and current in a load:

- Power dissipation:

$$P = V_{dc} I_{dc} = \frac{V_{dc}^2}{R} = I_{dc}^2 R$$

- With time-varying voltage, and hence the current, power will depend on waveforms
- RMS values help us calculate power of AC signals when signals are periodic
 - RMS voltages and currents useful for specifying and determining temperature rise of switching devices such as thyristors and diodes
 - For the circuit with AC signals, instantaneous load power:

$$P(t) = \frac{V_{ac}(t)^2}{R}$$

- Heating effect depends on average power over one period
- Integrate instantaneous power over the period and divide by period T :

$$P_{av} = \frac{1}{T} \int_{t_1}^{t_1+T} \frac{V_{ac}(t)^2}{R} dt$$

- Work with angle θ rather than t , where $\theta = \omega_0 t$, with ω_0 fundamental frequency:

$$t = \frac{\theta}{\omega_0} = \frac{\theta}{2\pi f_0} = \frac{\theta T}{2\pi}$$

$$dt = \frac{T}{2\pi} d\theta$$

- Hence

$$P_{av} = \frac{1}{2\pi} \int_{\theta_1}^{\theta_1+2\pi} \frac{V_{ac}(\theta)^2}{R} d\theta$$

- We now define the RMS voltage V_{RMS} as a DC voltage which when flowing in the load generates the same power as when the AC waveform is applied; hence:

$$P_{av} = \frac{1}{2\pi R} \int_{\theta_1}^{\theta_1+2\pi} V_{ac}(\theta)^2 d\theta = \frac{V_{RMS}^2}{R} = P_{dc}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\theta_1}^{\theta_1+2\pi} V_{ac}(\theta)^2 d\theta}$$

- V_{ac} is first squared, then we take mean of that over one period and finally we take square-root – hence name root-mean-square

- If we had worked with the current waveform, we would have obtained:

$$I_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\theta_1}^{\theta_1+2\pi} I_{ac}(\theta)^2 d\theta}$$

- For specific waveforms, ratio of RMS to peak values readily available
- For sine waves


$$I_{ac}(t) = I_m \sin \omega t \quad \text{and} \quad V_{ac}(t) = V_m \sin \omega t$$

- We can easily show, using the above equation, that:

$$I_{RMS} = \frac{I_m}{\sqrt{2}} \quad V_{RMS} = \frac{V_m}{\sqrt{2}}$$

$$P_{av} = V_{RMS} I_{RMS} = \frac{V_{RMS}^2}{R} = I_{RMS}^2 R$$

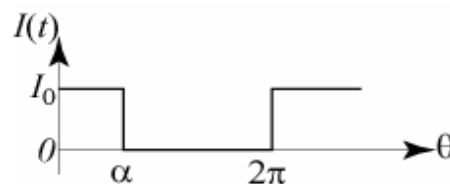- Typical current waveform encountered in power electronics:




- Using above equation to calculate RMS value of current:

$$I_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{\alpha} I_0^2 d\theta} = \sqrt{\frac{1}{2\pi} [I_0^2 \theta]_0^{\alpha}} = \sqrt{\frac{1}{2\pi} I_0^2 \alpha} = I_0 \sqrt{\frac{\alpha}{2\pi}}$$

- This is a very useful result that can be applied in many situations
- We now apply it to the 3-phase fully-controlled converter

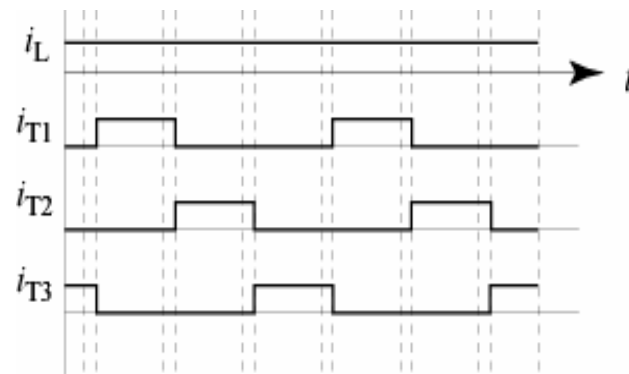- Thyristor RMS current of 3-phase half-wave fully-controlled converter



- Conduction angle is $\alpha = 2\pi/3$ and thyristor current $I_0 = I_L$

- RMS thyristor current:

$$I_{RMS} = I_0 \sqrt{\frac{\alpha}{2\pi}} = I_L \sqrt{\frac{2\pi/3}{2\pi}} = \frac{I_L}{\sqrt{3}}$$

Assuming constant load current

Example

- A 3-phase, half-wave, fully-controlled converter is connected to a 380V supply
- The load current is constant at 32A and is independent of firing angle
- Find the mean load voltage at firing angles of 0° and 45° , assuming that the thyristors have a forward voltage drop of 1.2V
- What will be the thyristor current and peak reverse voltage ratings?
- What will be the average power dissipation in each thyristor?

■ *Solution*

- When voltage of 3-phase system is specified it is usual to specify line voltage expressed as RMS quantity
- Multiply by $\sqrt{2}$ to convert from RMS to peak and divide by $\sqrt{3}$ to convert from line voltage to phase voltage

$$V_m = \frac{380 \times \sqrt{2}}{\sqrt{3}} = 310.3V$$

- For practical (non-ideal) thyristors and diodes, mean output voltage is reduced by device forward voltage drops
- Mean load voltage for half-wave 3-phase fully-controlled converter less thyristor forward voltage drop:

$$V_{mean} = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha - V_T = 256.6 \cos \alpha - 1.2$$

- For $\alpha = 0$:

$$V_{mean} = 256.6 \cos 0 - 1.2 = 255.4V$$

- For $\alpha = 45^\circ$:

$$V_{mean} = 256.6 \cos 45^\circ - 1.2 = 180.2V$$

- Ratings

We have:

$$I_{rms} = \frac{I_L}{\sqrt{3}} = \frac{32}{\sqrt{3}} = 18.47 A$$




- Peak reverse voltage (PRV) is equal to peak value of AC line voltage:

$$PRV = \sqrt{2}V_{line} = \sqrt{2} \times 380 = 537.4V$$

- Average power dissipation in thyristor is obtained by forming product of RMS voltage and current:

$$\begin{aligned} P_{av} &= v_{t(RMS)} i_{t(RMS)} \\ &= \frac{\hat{v}_t}{\sqrt{3}} \frac{I_L}{\sqrt{3}} = \frac{1.2 \times 32}{3} = 12.8 W \end{aligned}$$

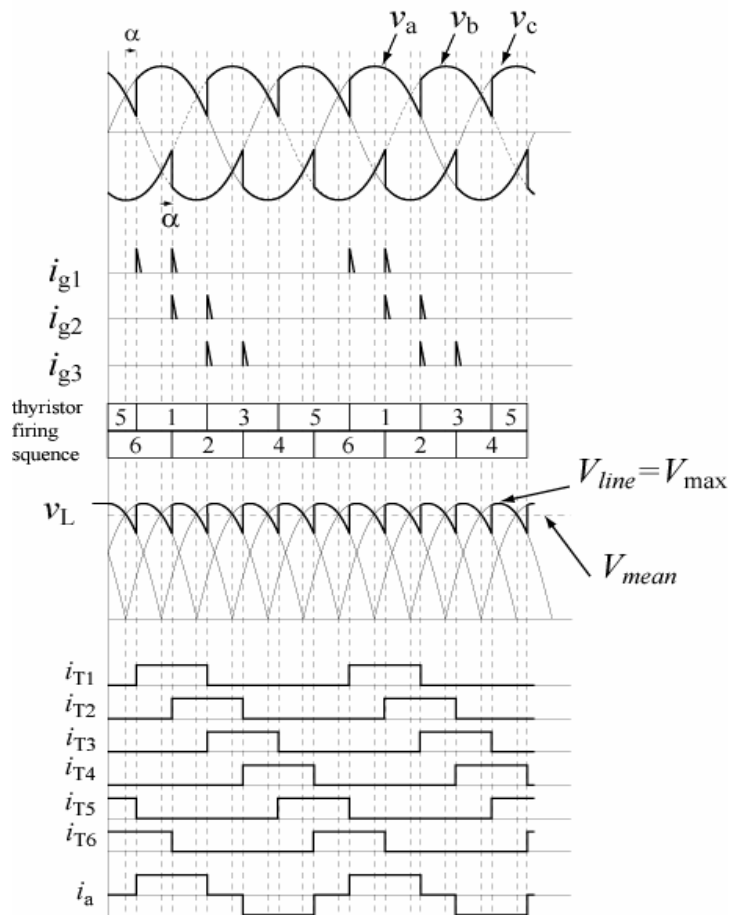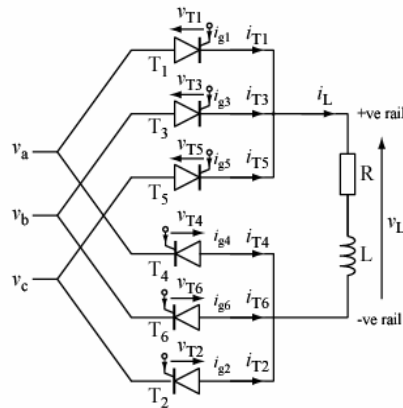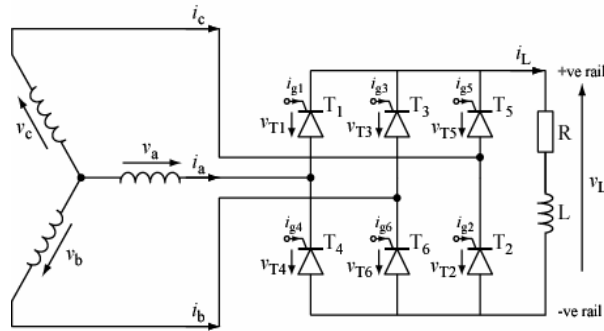
3-phase fully-controlled bridge converter




- 2 groups of 3 thyristors operate with conduction angle = 120°
- Each thyristor in lower group fired 60° after counterpart in upper group
- Load voltage = difference in output voltages of two groups
- Load voltage ripple period of $1/6^{\text{th}}$ supply period
- Pulse number = 6
- 6-pulse load voltage waveform provides lower values of load voltage and current ripple than the half-wave 3-phase converter (3-pulse)
- Pairs of thyristors (one in upper group and one in lower group) may be gated simultaneously to initiate operation of converter
- Each thyristor supplied with two firing signals 60° apart; second signal has no effect on thyristor once operation has been initiated and conduction sequence established

3-phase half-controlled bridge converter

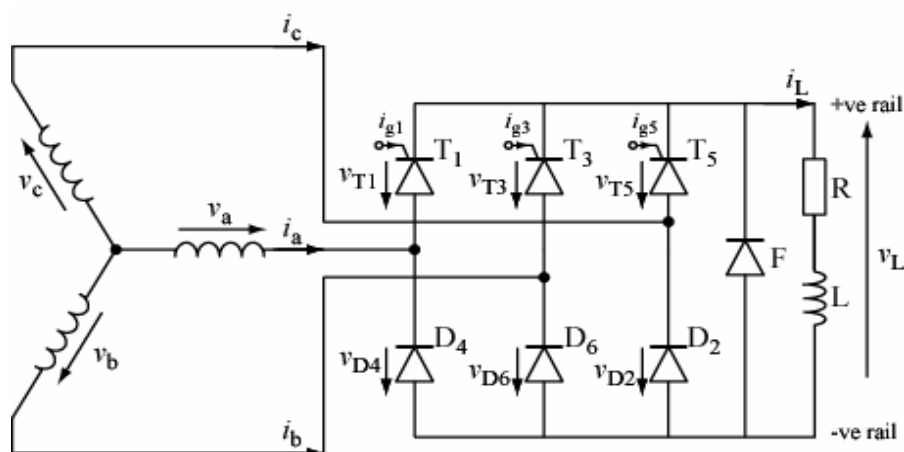- Replace 3 lower thyristors in 3-phase fully-controlled bridge converter by diodes and add a freewheeling diode:



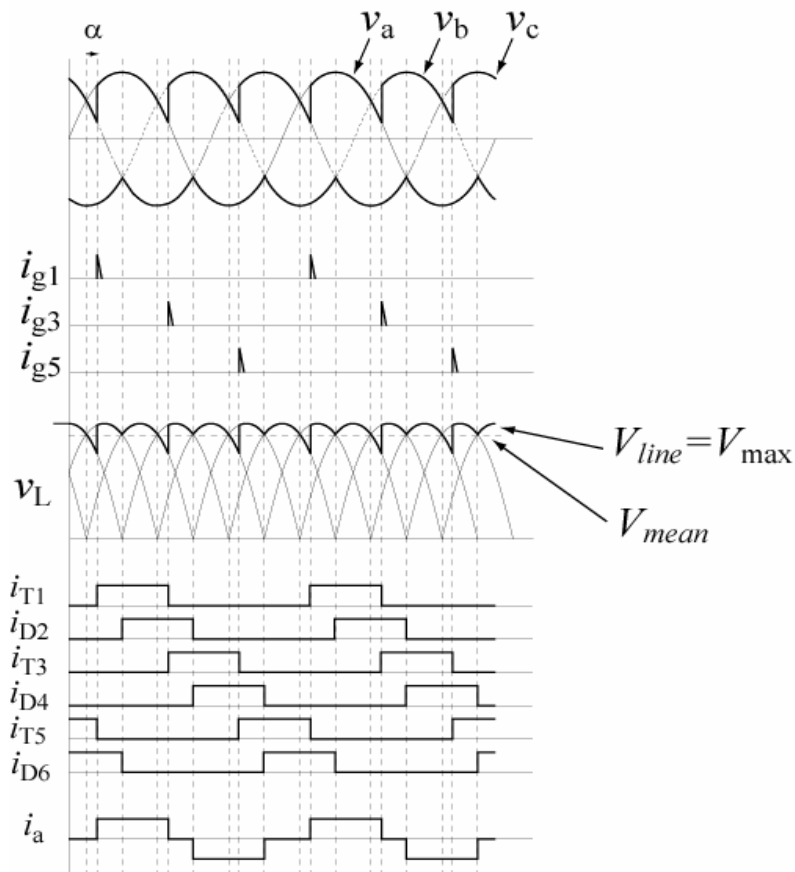

- Consider first operation of converter when firing angle α is $< 60^\circ$
- Denote positive and negative voltages on load as V_+ and V_-
- Load voltage given by

$$V_L = V_+ - V_-$$

- Assume value for α of about 30°
- Plot of V_+ and V_- and three phase voltages of the supply


- When a thyristor fires, V_+ switches to tracking next phase voltage
- V_- switches to next phase voltage as it becomes more negative than previous one
- Load voltage V_L always equal to a line voltage
- Load voltage switches from one line voltage to another
- For $0 \leq \alpha \leq 60^\circ$, instantaneous load voltage is always positive and commutating diode plays no part in the operation of the converter

- Mean load voltage for $0 \leq \alpha \leq 60^\circ$ can be calculated by integrating appropriate sections of the line voltage waveforms:

$$V_{mean} = \frac{3}{2\pi} \left[\underbrace{\int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin \theta d\theta}_{\text{upper track}} + \underbrace{\int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} V_m \sin \theta d\theta}_{\text{lower track}} \right] = \frac{3}{2\pi} V_m (1 + \cos \alpha)$$

- V_m is peak value of supply line voltage = $\sqrt{2} \times V_{line(RMS)}$
- Maximum firing angle for this mode $0 < \alpha < 60^\circ$

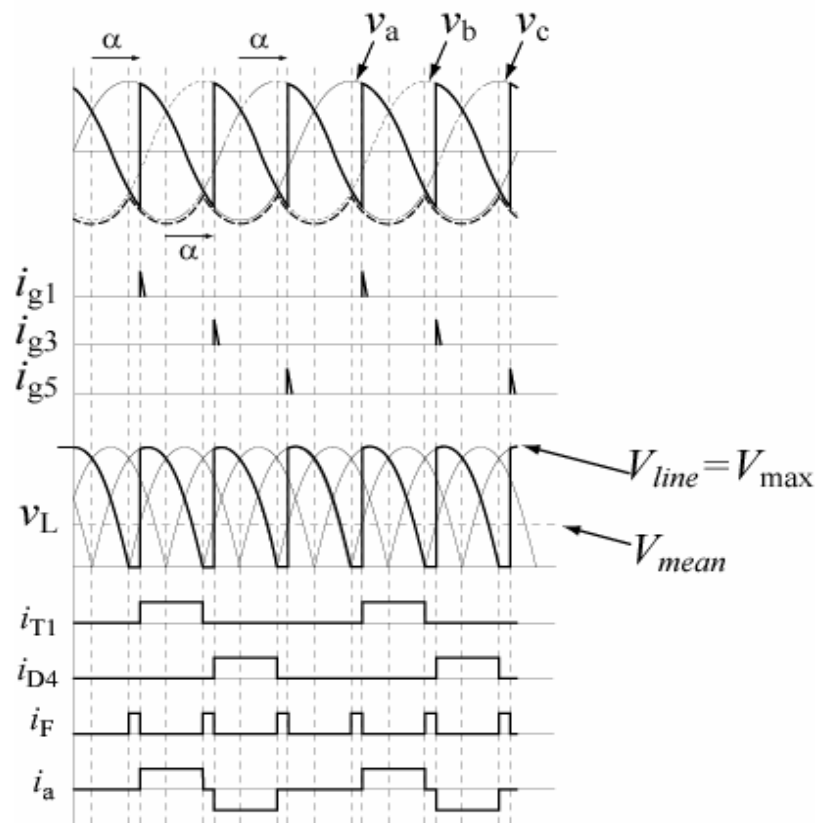- Plot of V_+ and V_- waveforms for $\alpha \approx 90^\circ$:
 - When firing angle reaches 60° , V_+ would become equal to V_- and hence load voltage would attempt to become negative
 - Freewheeling diode becomes conducting and takes load current during this part of cycle
 - Maximum firing angle for this mode is $\alpha = 120^\circ$



- Mean load voltage for $60 \leq \alpha \leq 120^\circ$ can be calculated by integrating appropriate section of line voltage waveform:

$$\begin{aligned} V_{mean} &= \frac{3}{2\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta \\ &= \frac{3}{2\pi} V_m (1 + \cos \alpha) \end{aligned}$$

Same expression as for $0 \leq \alpha \leq 60^\circ$

- For $\alpha > 60^\circ$, half-controlled converter output voltage waveform changes from 6-pulse waveform to 3-pulse waveform, losing key advantage of the 3-phase bridge converter

Summary

- Have examined simplified ideal operation of naturally commutated converters
- Considered operation of uncontrolled, fully-controlled and half-controlled converters
- Developed general equations describing converter behaviour
- Converters for single phase half-wave and full-wave supplies as well as 3-phase supplies were analysed
- For converters considered, we calculated key performance parameters including converter mean output voltage and thyristor peak reverse voltage and RMS current