

Lecture 6

Converters IV – Design aspects


1

Objectives


- We consider problem of transformer magnetising current and how this can be solved by special transformer winding schemes
- In order to reduce load voltage ripple, we consider converters with higher pulse numbers of 6 and 12; techniques include use of star and delta connected transformer windings
- We also consider miscellaneous converter topics including regulation, power factor, transformer ratings, discontinuous supply current and converters driving loads with voltage bias

Transformer supply and magnetising current

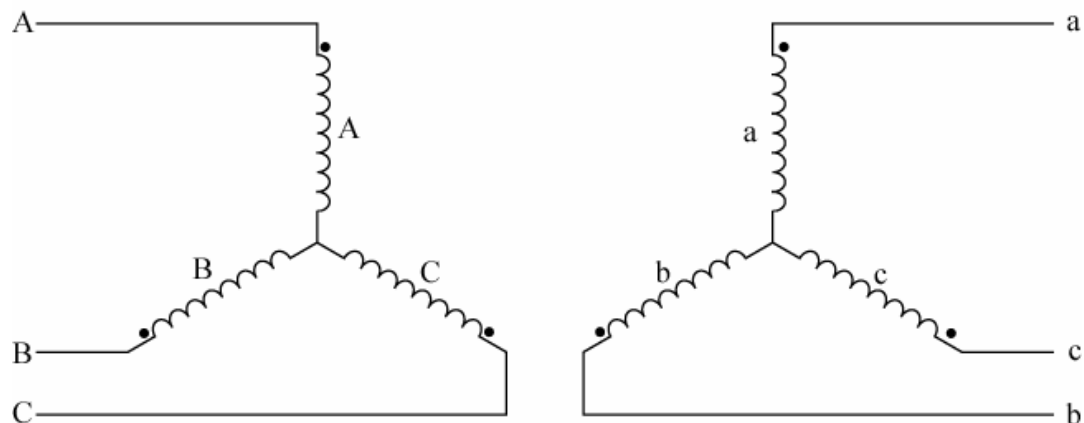- In practice, converter is often connected to supply via transformer
- Star-star transformer:



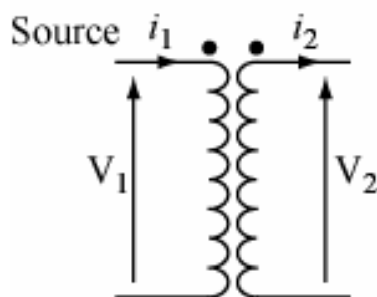
- 3-phase transformer – 3 single phase transformers; primary windings A, B, C; secondary windings a, b and c
- Dot convention used with mutually coupled coils:



- Voltage in coupled coil has polarity indicated


- When 3-phase transformer is used to supply 3-phase converter, current in each transformer secondary is identical to current in thyristor to which it is connected, which is unidirectional
- Currents in primary windings will also be unidirectional
- DC magnetisation of transformer core – deterioration in transformer performance
- In order to prevent magnetisation of the transformer core, the interconnected star secondary winding may be used

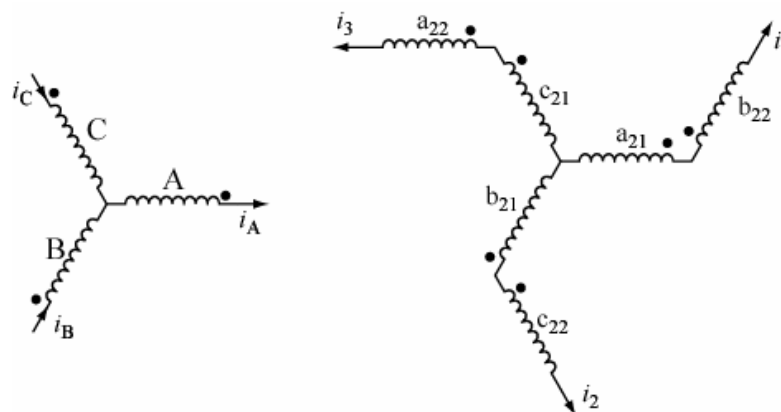- Interconnected star secondary winding arrangement:



- For each phase transformer, there are 3 windings; e.g. for phase A, A is primary winding and a_{21} and a_{22} are secondary windings
- Diagrams show electrical interconnections and also vector relationships of winding voltages; e.g. primary windings are arranged at relative angles of 120° ; secondary windings a_{21} and a_{22} are drawn parallel to their primary winding (A) and with correct polarity relationship

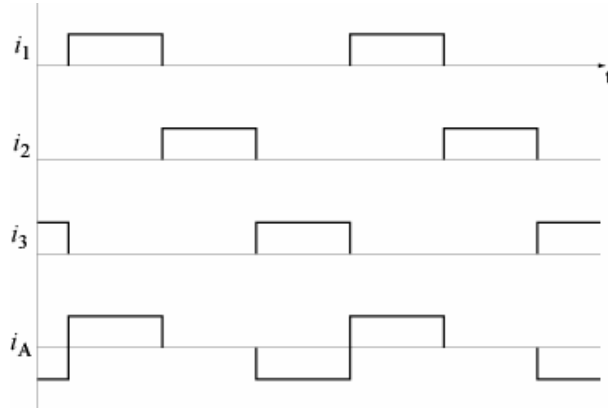
- Thyristor currents i_1 , i_2 and i_3 and one AC supply currents i_A




- i_1 causes a positive supply current and i_3 a negative supply current
- Interconnected star arrangement ensures bi-directional current in each transformer primary

Converters with higher pulse numbers 6-pulse systems

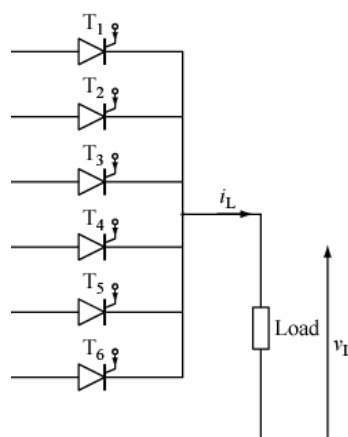- Increasing pulse number reduces output voltage ripple
- We have already looked at 3-phase bridge converter (fully controlled and half-controlled) which has a 6-pulse output waveform
- Consider the 6-phase half-wave converter:




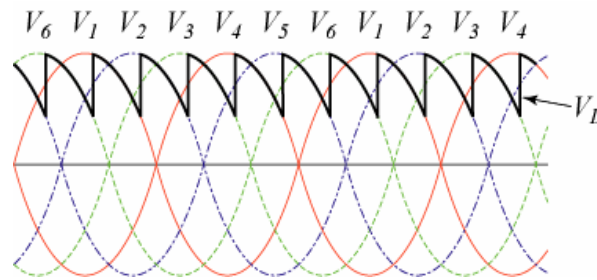- Thyristor driven from 6-phase supply
- Supply waveforms and output voltage for $\alpha \approx 30^\circ$:



- Thyristors conduct for $1/6^{\text{th}}$ supply period, i.e. conduction angle = 60°

- Arrangement for 6-phase supply:

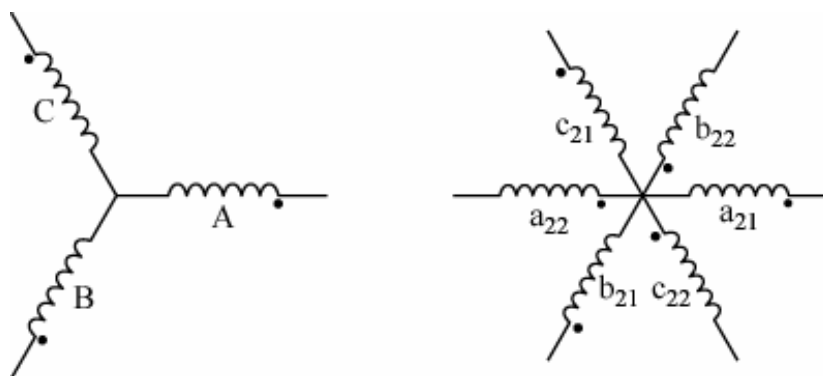


- Converter ground return from load connected to mid-point of secondary 3-phase full-wave or 6-phase half-wave converter with 3-phase supply

- No magnetising current problems since two secondary windings for each phase make primary winding currents are bi-directional
- Current flows in each primary winding for only two 1/6ths (1/3rd) cycle
- High levels of harmonic currents in primary circuit

▪ Star-fork connection

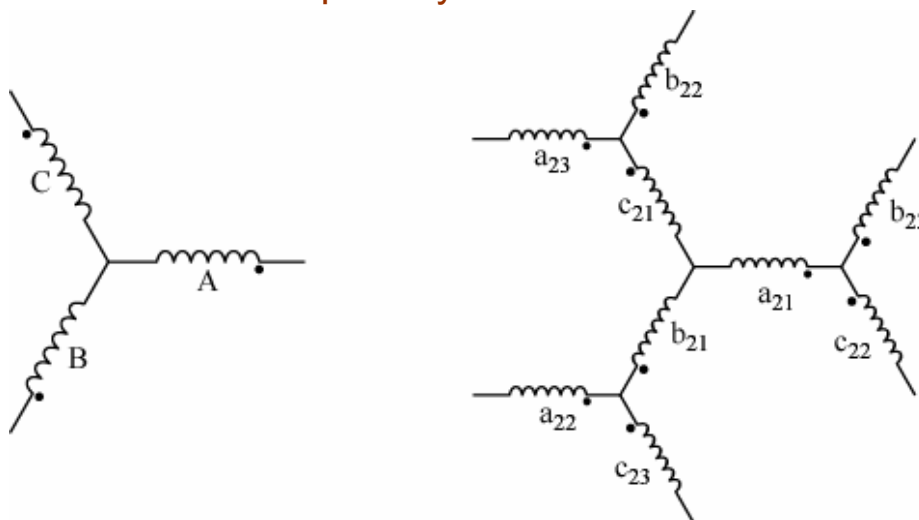
- Reduced level of primary harmonic current



- Current flows in each phase of the primary winding for 2/3rds cycle
- 3rd-harmonic current in primary is zero


- Dual converter arrangement

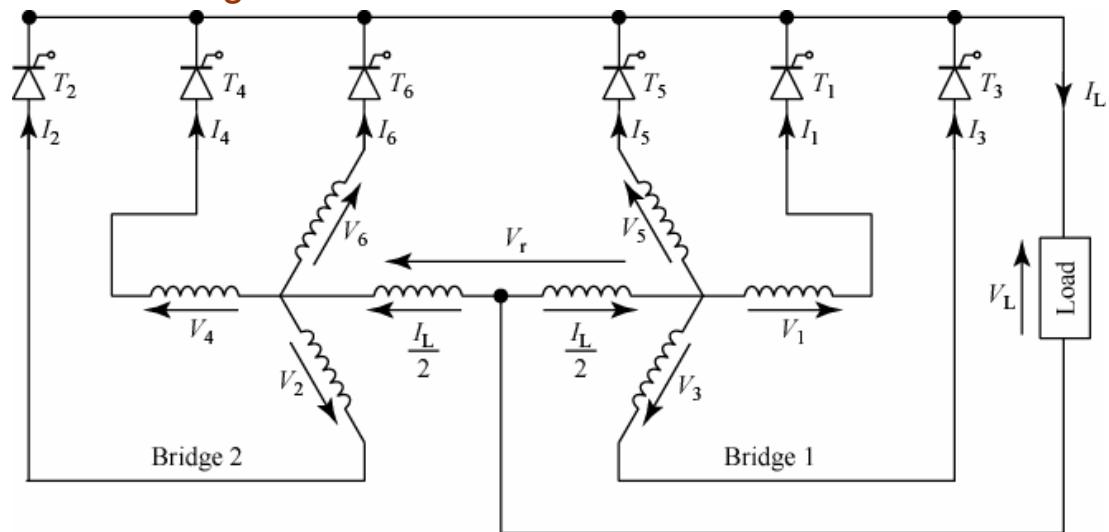- Reduces cost associated with complex transformer windings:




- Each group (T_1, T_3, T_5 and T_2, T_4, T_6) – 3-phase, half-wave bridge – each thyristor conducts for 120°

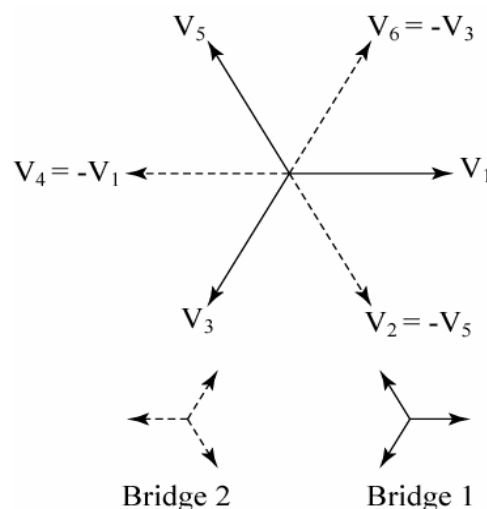- Secondary windings for each bridge have opposite polarity and therefore output voltage ripple transients for each converter are phase shifted with respect to each other by 60° :




- Star points of two secondary windings of supply transformer are connected by interphase reactor

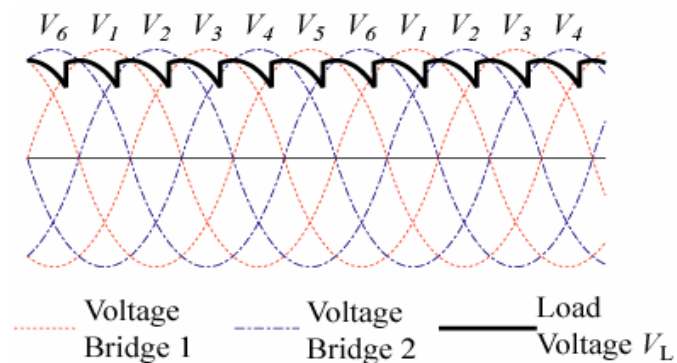- Load voltage is mean of output voltages of individual 3-phase, half-wave groups:



- Load voltage ripple period is $1/6^{\text{th}}$ of supply period $\therefore p = 6$

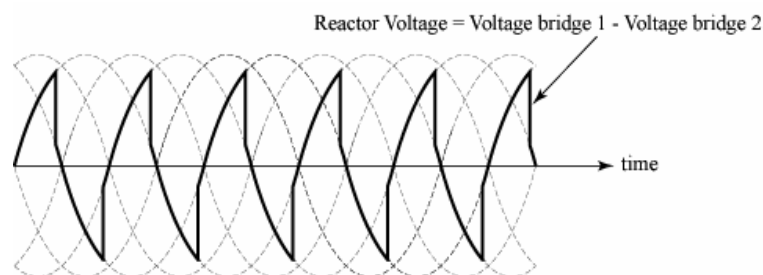- Potential difference across interphase reactor is the difference between the output voltages of individual 3-phase, half-wave converters




- Operations of interphase reactor depends on presence of circulating magnetising current which flows between two star points with return path via conducting thyristors of each group
- For magnetising current to flow, load current must be $>$ magnetising current

- Therefore often operated into permanently connected load
- 6-pulse systems using 6-phase half-wave converter and dual converter with interphase reactor both relatively inefficient in terms of need for special transformers and additional inductive reactors
- The 3-phase bridge configurations considered already provide 6-pulse output without need for transformers or reactors


12-pulse systems

- Pulse numbers > 6 are needed to further reduce load voltage ripple
 - e.g. high-voltage DC (HVDC) power transmission systems
- Basic 3-phase system has phase voltages which differ in phase by 120°
- 3-phase transformer gives 6 phase voltages differing in phase by 60°

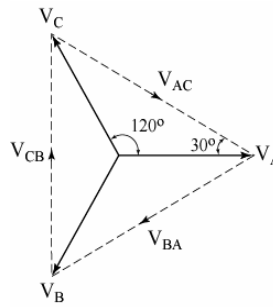
- Line voltages in 3-phase system (V_{AC} , V_{BA} and V_{CB}) are differences between 3 phase voltages:



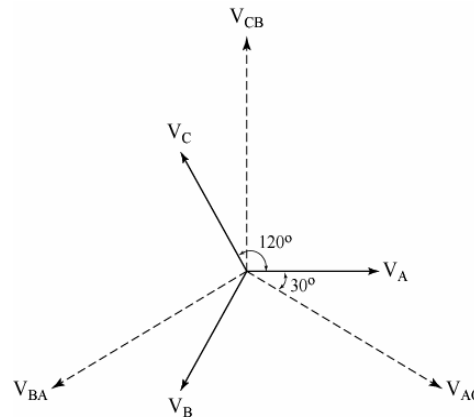- Differ from each other by 120° ; shift = 30° in relation to phase voltages:



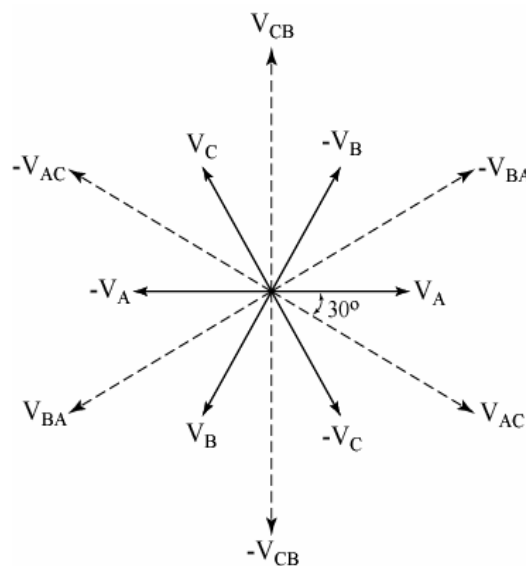
- Line and phase voltages with reversed polarity:



- 12-phase half-wave system – 30° phase difference between each phase; also described as 6-phase full-wave system


- Line voltages larger than magnitude of phase voltages by $2\cos 30^\circ = \sqrt{3}$
- Line voltages – from 3-phase supply with conventional 3-phase transformer with primary windings delta-connected
- Second transformer with star-connected primary with provide phase voltages
- Each transformer – two secondary windings for opposite polarity voltages
- Turns ratio of delta-connected transformer can be adjusted so that line voltages and phase voltages from two transformers have same magnitude

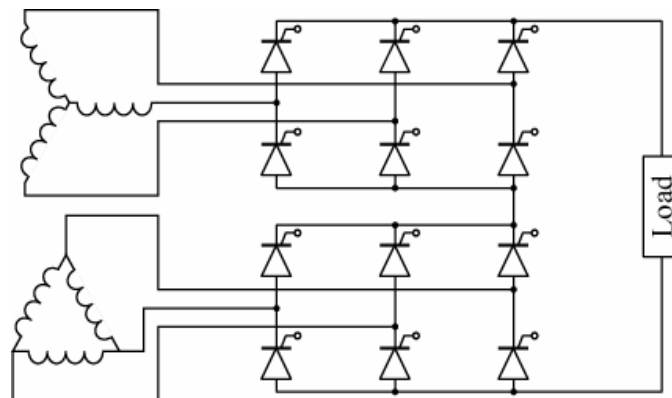▪ 12 pulse converter using two 6-pulse bridges



- One bridge fed with phase voltages and one with line voltages
- Combined by connecting them in series
- Each converter is bridge converter with 60° phase shift between its upper and lower thyristor group
- Hence period of load voltage ripple is $1/12^{\text{th}}$ of supply period

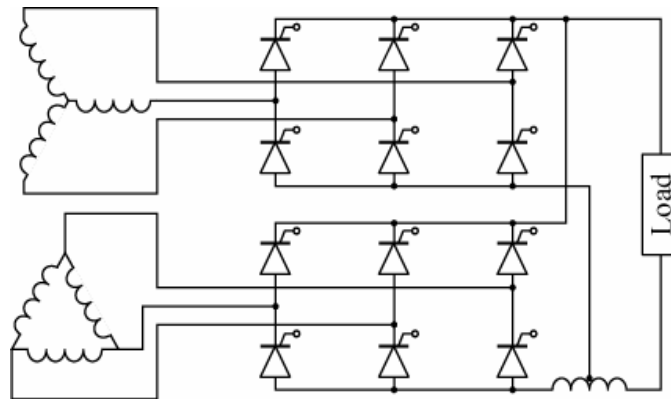- Instead of combining outputs of two converters by connecting their outputs in series, they may be interconnected using a centre-tapped transformer:




Worked Example On High Pulse Number Converters

- Two AC supply systems are interconnected by a DC link via two 6-pulse, fully-controlled bridge converters, each consisting of two 3-phase converters with interphase reactor
 - The DC transmission line has a resistance of 0.2Ω
 - Of the two 3-phase AC systems one is 415V (line), 50 Hz and the other 380V (line), 60 Hz
 - Source inductance of the 50 Hz system is 1 mH per phase
 - Source inductance of the 60 Hz system is 1.25 mH per phase
 - If the DC link is carrying a constant DC current of 50A and delivering 15 kW into the 60 Hz system, find the firing advance angle and the firing angle of the two converters

- **Solution**

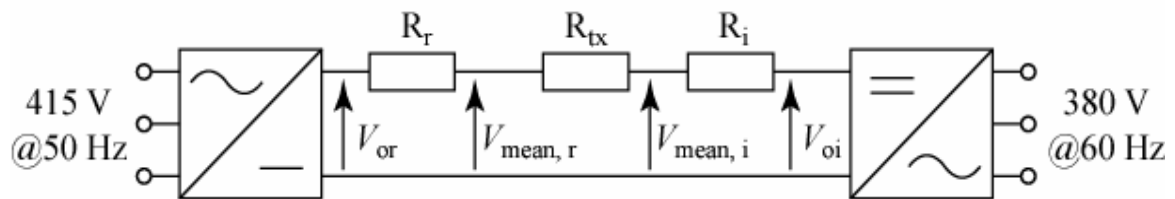- The equivalent circuits for the two converters, one in converting mode and one in inverting mode, can be combined with the DC link resistance to give the system equivalent circuit



- The values of R_r and R_i can then be calculated from the previous expressions and the given data

$$R_r = \frac{p\omega L_{(50\text{Hz})}}{2\pi} = \frac{6 \times 2\pi \times 50 \times 10^{-3}}{2\pi} = 0.3\Omega$$

$$R_i = \frac{p\omega L_{(60\text{Hz})}}{2\pi} = \frac{6 \times 2\pi \times 60 \times 1.25 \times 10^{-3}}{2\pi} = 0.45\Omega$$

- The mean voltage for the converter in the inverter-mode can be found from the power flow and DC current:

$$V_{mean(i)} = \frac{15000}{50} = 300V$$

- The mean voltage in the absence of overlap can then be found:

$$V_{0(i)} = V_{mean(i)} - R_i I_L = 300 - 50 \times 0.45 = 277.5V$$

- The mean load voltage of the inverter-mode converter is given by

$$V_{0(i)} = \frac{p}{\pi} V_{m(i)} \sin\left(\frac{\pi}{p}\right) \cos \beta$$

$$\begin{aligned} \cos \beta &= \frac{V_{0(i)}}{V_{m(i)}} \frac{\pi}{p \sin(\pi/p)} = \frac{277.5 \times \pi}{380 \times \sqrt{2} \times 6 \times \sin 30^\circ} \\ &= 0.5408 \\ \beta &= 57.26^\circ \end{aligned}$$

- The mean voltage for the converter in the converter-mode can be found

$$V_{mean(r)} = V_{mean(i)} + R_t I_L = 300 + 0.2 \times 50 = 310V$$

- The mean voltage in the absence of overlap can then be found:

$$V_{0(r)} = V_{mean(r)} + R_r I_L = 310 + 0.3 \times 50 = 325V$$

- The mean load voltage of the converter-mode converter is given by

$$V_{0(r)} = \frac{p}{\pi} V_{m(r)} \sin\left(\frac{\pi}{p}\right) \cos \alpha$$

$$\cos \alpha = \frac{V_{0(r)}}{V_{m(r)}} \frac{\pi}{p \sin(\pi/p)} = \frac{325 \times \pi}{\frac{415}{\sqrt{3}} \times \sqrt{2} \times 6 \times \sin 30^\circ} = 0.5799$$

$$\alpha = 54.56^\circ$$


Regulation

- Device voltage drops, device forward resistance, conductor resistance and overlap (due to AC supply inductance), cause on-load output voltage V_{load} of converter to differ from ideal source voltage V_{OC}
- Difference expressed by regulation:

$$\text{Regulation} = \frac{V_{oc} - V_{load}}{V_{oc}} \times 100\%$$

- Voltage drop across diode or thyristor may be represented by constant voltage, combination of constant voltage and resistance

- Typical equivalent circuit:

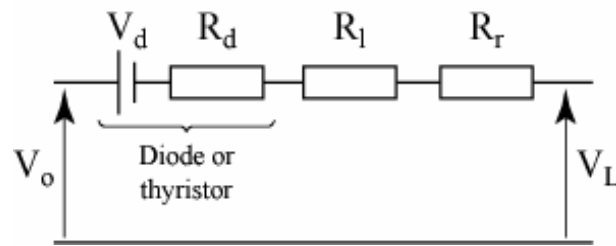

- Parameters:
 - V_d = device voltage drop
 - R_d = device resistance
 - R_l = lead resistance
 - R_r = effective resistance due to overlap
- Precise values used must take account of firing angle

- Resistance of leads and AC source can be taken as constant
- Where bridge operation causes current to flow in two phases simultaneously, effective AC source resistance in equivalent circuit will be sum of phase resistances

Power factor

- General expression:

$$\text{Power factor} = \frac{\text{Mean power}}{V_{RMS} I_{RMS}} = \frac{\frac{1}{T} \int_0^t v i dt}{V_{RMS} I_{RMS}}$$

- Converters draw non-sinusoidal current at supply frequency from AC system
- Current can be represented by fundamental component at supply frequency together with series of harmonics

- Assuming AC system voltage remains sinusoidal, there will be no power associated with current harmonics and power will be delivered by AC system at fundamental frequency only; therefore

$$\text{Mean power} = V_{1,RMS} I_{1,RMS} \cos \phi_1$$

- $I_{1,RMS}$ is RMS amplitude of fundamental component of AC system current
- $V_{1,RMS}$ is RMS amplitude of fundamental component of AC system voltage;
- ϕ_1 is phase angle between $V_{1,RMS}$ and $I_{1,RMS}$ (also referred to as phase displacement)
- Also, we have: $V_{1,RMS} = V_{RMS}$ (for an undistorted sinewave)

- $$I_{RMS} = \left[I_{1,RMS}^2 + I_{2,RMS}^2 + I_{3,RMS}^2 + \dots \right]^{\frac{1}{2}}$$

- Hence, we obtain:

$$\text{Power factor} = \frac{V_{1,RMS} I_{1,RMS} \cos \phi_1}{V_{1,RMS} I_{RMS}} = \frac{I_{1,RMS} \cos \phi_1}{I_{RMS}} = \mu \cos \phi_1$$

- Where

$$\mu = I_{1,RMS} / I_{RMS}$$

is referred to as current distortion factor

- $\cos \phi_1$ as displacement factor
- Whenever harmonic currents are present then distortion factor μ will be < 1 , even if fundamental components of current and voltage are in phase ($\cos \phi_1 = 1$)
- For fully-controlled converter with constant load current, then ϕ_1 will be equal to firing angle α if we ignore overlap.

- Situation for half-controlled converter is more complicated and reference must be made to relevant AC current waveforms


Worked Example On Power Factor

Part 1

- Find the power factor for a fully-controlled, single-phase bridge converter at firing angles of 30° and 60°
- Overlap and device forward voltage drops can be ignored and the load current is assumed to be constant

Solution

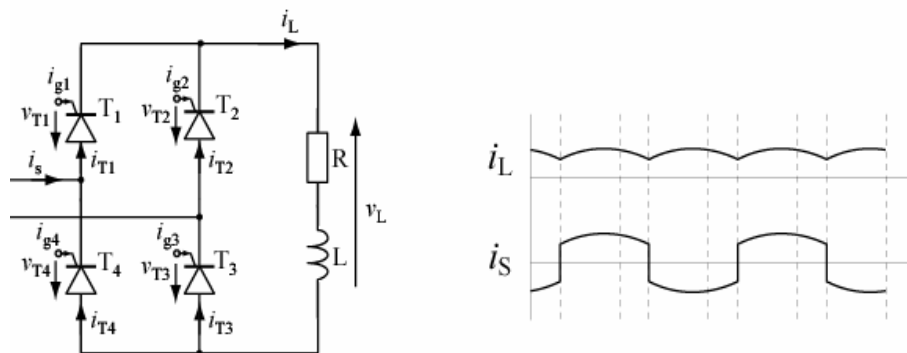- The circuit diagram of the fully-controlled, single-phase bridge converter and its load and supply current are as follows:



- Mean load voltage given by:

$$V_{mean} = \frac{2}{\pi} V_m \cos \alpha = \frac{2\sqrt{2}}{\pi} V_{RMS} \cos \alpha$$

- Assume load current constant:

- Mean load power is $V_{mean}I_L$ and power factor is:

$$PF = \frac{V_{mean}I_L}{V_{RMS}I_{RMS}} = \frac{2\sqrt{2}}{\pi} \cos \alpha$$

- Since the load current is assumed constant and overlap is ignored, $\cos \phi_1 = \cos \alpha$
- Also,


$$\mu = \frac{I_{1,RMS}}{I_{RMS}} = \frac{2\sqrt{2}}{\pi} = 0.9003$$

- Independent of firing angle
- For $\alpha = 30^\circ$
Power factor = 0.7797
- For $\alpha = 60^\circ$
Power factor = 0.4502

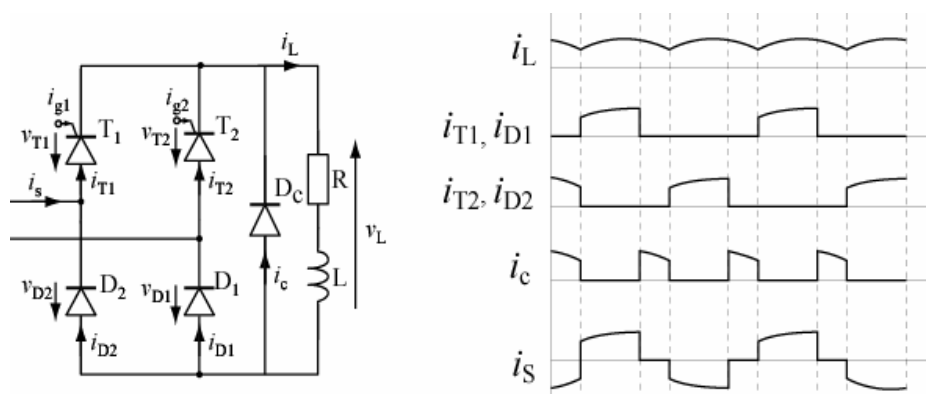Part 2

- Find the power factor for a half-controlled, single-phase bridge converter for firing angles of 30° and 60°
- Solution**

Circuit diagram of half controlled, single-phase bridge converter and its load and supply current are:



- Mean load voltage:

$$V_{mean} = \frac{1}{\pi} V_m (1 + \cos \alpha) = \frac{\sqrt{2}}{\pi} V_{RMS} (1 + \cos \alpha)$$

- Thyristor current and supply current discontinuous:
- RMS current:

$$I_{RMS} = \left[\frac{1}{\pi} \int_{\alpha}^{\pi} I_L^2 d\theta \right]^{1/2} = I_L \left[\frac{\pi - \alpha}{\pi} \right]^{1/2}$$

- Mean load power is then $V_{mean} I_L$ and power factor is:

$$PF = \frac{\sqrt{2}}{\pi} (1 + \cos \alpha) \left(\frac{\pi}{\pi - \alpha} \right)^{1/2}$$

- By Fourier analysis, sine and cosine Fourier coefficients for the fundamental component of current are:

$$b_1 = \frac{1}{\pi} \left[\int_{-(\pi-\alpha)}^0 -I_L \sin \theta d\theta + \int_{\alpha}^{\pi} I_L \sin \theta d\theta \right] = \frac{2}{\pi} I_L (1 + \cos \alpha)$$

$$a_1 = \frac{1}{\pi} \left[\int_{-(\pi-\alpha)}^0 -I_L \cos \theta d\theta + \int_{\alpha}^{\pi} I_L \cos \theta d\theta \right] = \frac{2}{\pi} I_L \sin \alpha$$

- Amplitude of fundamental current component:

$$\hat{I} = (a_1^2 + b_1^2)^{1/2} = \frac{2\sqrt{2}}{\pi} I_L (1 + \cos \alpha)^{1/2}$$

- RMS value of fundamental current component:

$$I_{RMS} = \frac{2}{\pi} I_L (1 + \cos \alpha)^{1/2}$$

- Hence

$$\mu = \frac{2}{\pi} \left(\frac{\pi}{\pi - \alpha} \right)^{1/2} (1 + \cos \alpha)^{1/2}$$

- From expression for power factor we obtain:

$$\cos \phi_1 = \frac{1}{\sqrt{2}} (1 + \cos \alpha)^{1/2}$$

- For $\alpha = 30^\circ$

$$\mu = 0.9526 \quad \cos \phi_1 = 0.9659 \quad \text{Power factor} = 0.9201$$

- For $\alpha = 60^\circ$

$$\mu = 0.8541 \quad \cos \phi_1 = 0.866 \quad \text{Power factor} = 0.7397$$

Transformer rating


- When selecting transformers their rating under particular operating conditions must be determined
- Rating will in many cases be different for primary and secondary windings
- In normal transformer operation rating will be same for both windings
- Rating of a winding is obtained as product of RMS current through winding and RMS voltage across winding


Worked Example On Transformer Ratings

- 3-phase, half-wave, uncontrolled converter is supplying constant current of 25 A at 240 V to load
- Converter is supplied from secondary of interconnected star transformer, primary of which is connected to 3-phase, 660 V (line) supply
- Find ratings of transformer primary and secondary windings

▪ *Solution*

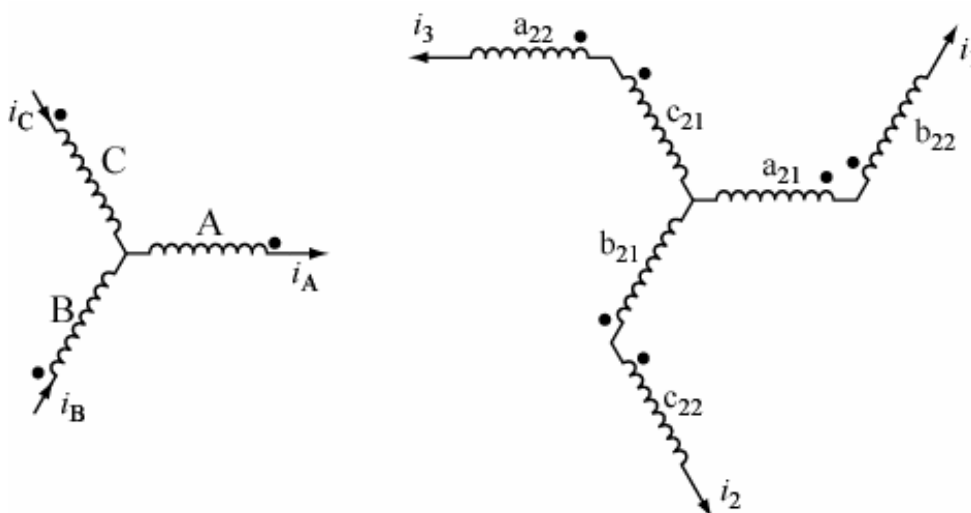- 3-phase uncontrolled converter + interconnected star transformer drive:



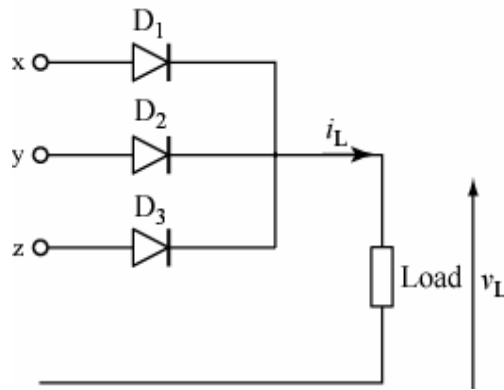


$$V_{mean} = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha \Big|_{\alpha=0} = \frac{3\sqrt{3}}{2\pi} V_m$$

- V_m is peak phase voltage of AC supply at transformer secondary

$$V_m = \frac{2\pi}{3\sqrt{3}} V_{mean} = \frac{2\pi}{3\sqrt{3}} 240 = 290.2 V$$

$$V_{RMS} = \frac{290.2}{\sqrt{2}} = 205.2 V$$

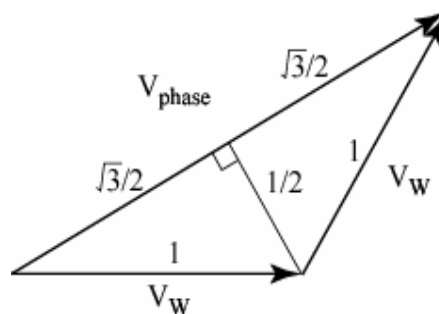- In interconnected star, each secondary phase voltage is developed as vector of two secondary winding voltages V_w :



- It follows from geometry that $V_{phase} = \sqrt{3}V_w$
- RMS winding voltage:

$$V_{W.RMS} = \frac{V_{RMS}}{\sqrt{3}} = \frac{205.2}{\sqrt{3}} = 118.4 V$$

- Load current I_L flows for 1/3rd of cycle in each transformer secondary; RMS secondary current:

$$I_{2.RMS} = \left(\frac{1}{3} I_L^2 \right)^{1/2} = \frac{I_L}{\sqrt{3}} = \frac{25}{\sqrt{3}} = 14.43 A$$

- Primary winding (phase) voltage is obtained from line voltage:

$$V_{1.RMS} = \frac{V_{line}}{\sqrt{3}} = \frac{660}{\sqrt{3}} = 381 V$$

- Turns ratio between primary winding and associated secondary windings:

$$R = \frac{n_p}{n_s} = \frac{V_{1.RMS}}{V_{W.RMS}} = \frac{381}{118.4} = 3.218$$

- Primary current amplitude:

$$I_1 = \frac{25}{3.218} = 7.77 A$$

- Primary current flows for 2/3rds of cycle
∴ RMS primary current:

$$I_{1.RMS} = \left(\frac{2}{3} I_L^2 \right)^{1/2} = \frac{\sqrt{2}}{\sqrt{3}} I_1 = \frac{\sqrt{2}}{\sqrt{3}} 7.77 = 6.34 A$$

- Transformer ratings:

Primary


$$P_p = 3 \times 6.34 \times 381 = 7.25 \text{ kW}$$

Secondary

$$P_s = 6 \times 14.43 \times 118.4 = 10.2 \text{ kW}$$

Converters with discontinuous current

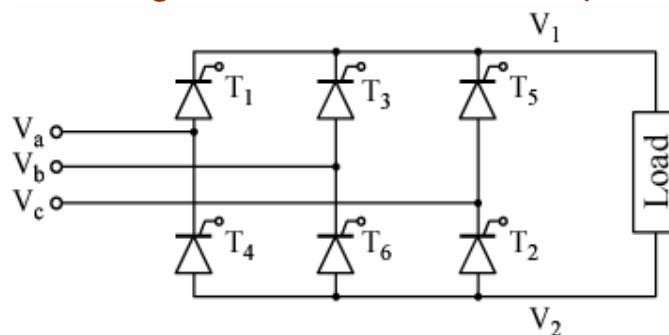
- Where load inductance is insufficient to maintain DC current constant, output current will contain a ripple component which will appear in supply current
- e.g. 6-pulse bridge converter fed from 3-phase supply




5	1	3	5	1	3	5
6	2	4	6	2	4	6

- Current flows in phase A of AC supply when T_1 or T_4 are conducting

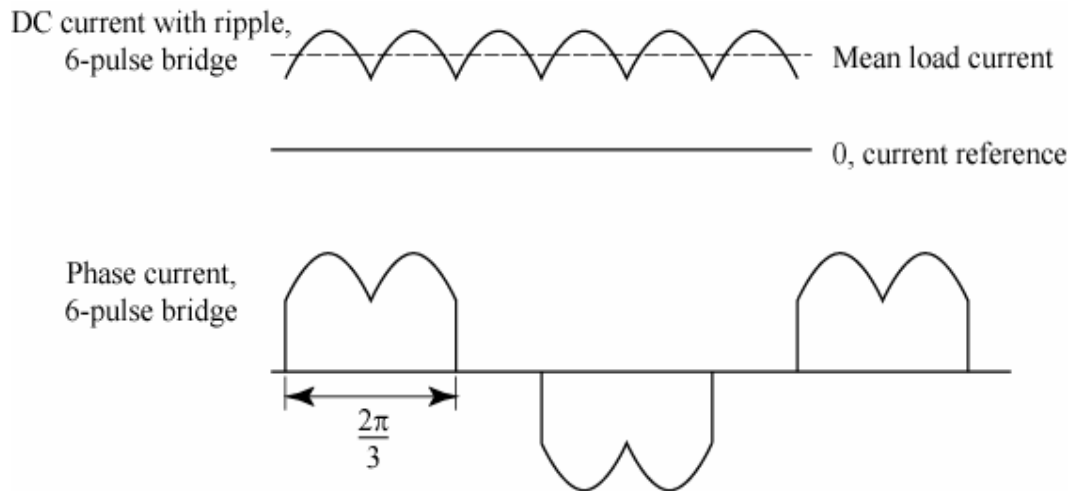
- Load current and phase A supply current when load current has significant ripple:




- Under light load conditions:

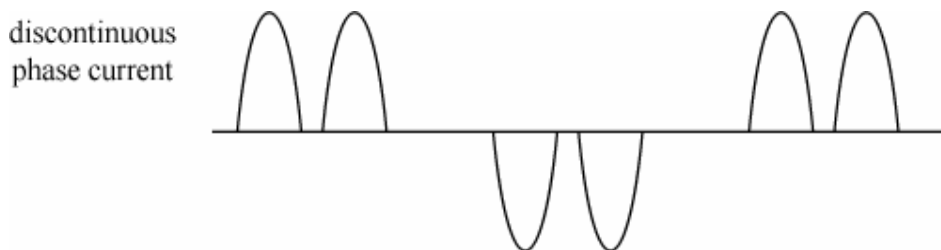

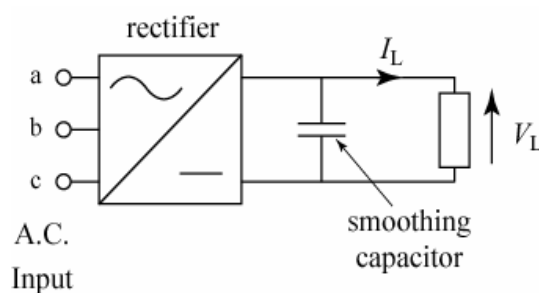
- Amplitude of current ripple exceeds mean load current
- Analysis of converter is much more complex in this case
- Capacitor smoothing of an uncontrolled converter (or rectifier) can make supply current discontinuous:



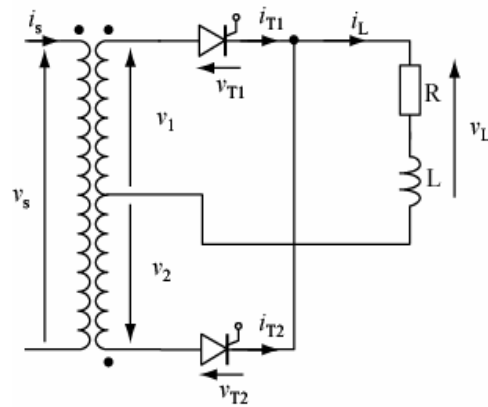- e.g. 2-phase, half-wave bridge with capacitor smoothing:



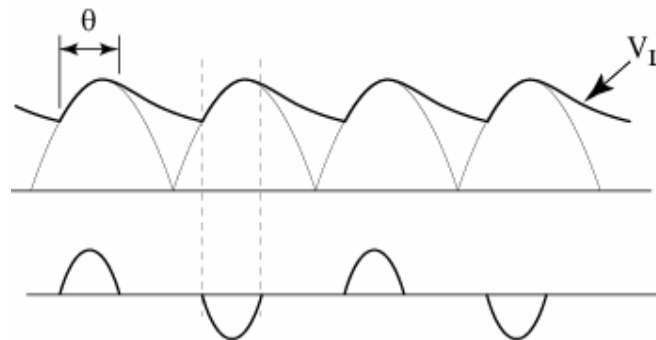- Diodes conduct once AC voltage at anode exceeds capacitor voltage:




- Conduction period θ can be approximated as:

$$\theta = 2 \cos^{-1} \left(\frac{V_{mean}}{V_m} \right)$$

- V_m is peak value of AC supply at transformer secondary


Converters with voltage bias

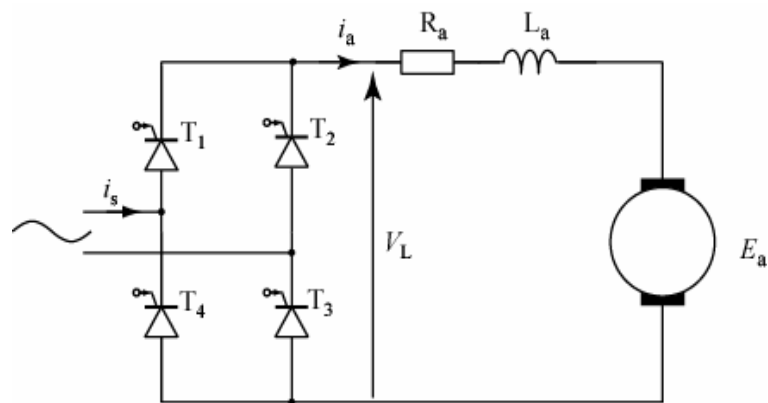- Consider fully-controlled converter supplying DC motor load:



- Back EMF of motor appears as bias voltage E_a on DC side of converter

- Supply voltage and load voltage:

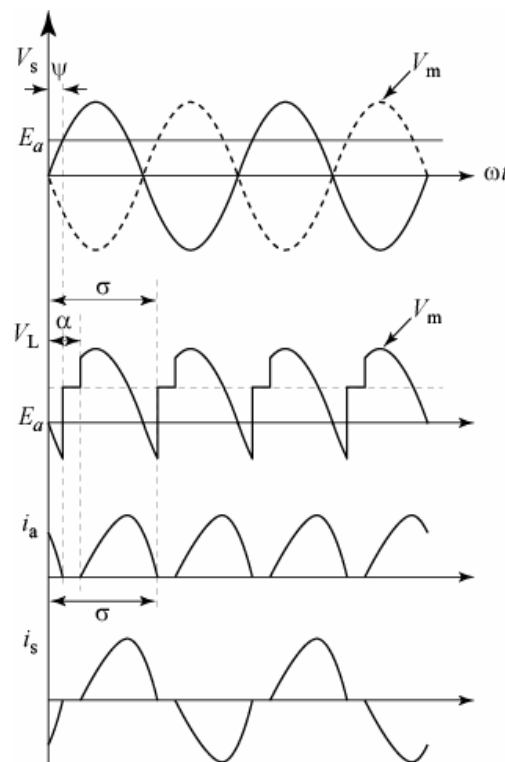

- α – firing angle of the thyristors
- ψ - point-on-wave at which AC source voltage exceeds bias voltage
- σ - point-on-wave when same zero of AC supply voltage
- α , ψ and σ all measured from same zero of AC supply voltage
- Performance of converter under these conditions depends on relationship between parameters
- Thyristors cannot be fired for $\alpha < \psi$
- Effective load voltage:

$$v_L = V_m \sin \theta \quad \text{for } \alpha < \theta < \sigma$$

$$v_L = E_a \quad \text{for } \sigma - \pi < \theta < \alpha$$

- Mean load voltage:

$$v_{mean} = \frac{1}{\pi} \left[\int_{\sigma - \pi}^{\alpha} E_a d\theta + \int_{\alpha}^{\sigma} V_m \sin \theta d\theta \right]$$

$$= \frac{1}{\pi} [V_m (\cos \alpha - \cos \sigma) + E_a (\alpha + \pi - \sigma)]$$

- Supply current becomes discontinuous:

Summary

- Have concluded topic of converters by considering some advanced design aspects:
 - Problem of transformer magnetising current
 - Development of converters with higher pulse numbers of 6 and 12
 - Other important topics including power factor and regulation
- Next we consider alternative class of systems in which natural commutation can not be used and we have to provide forced commutation
- This includes important classes of circuit, such as:
 - DC choppers
 - Inverters